

Announcements

▣ Homework for tomorrow...

Ch. 31: CQ 3, Probs. 1, 6, & 8

CQ10: a) doubles b) unchanged c) unchanged d) doubles

30.18: $\tau_{Al} = 2.1 \times 10^{-14} \text{ s}$, $\tau_{Fe} = 4.3 \times 10^{-15} \text{ s}$

30.20: a) 10 V/m b) $6.7 \times 10^6 \text{ A/m}^2$ c) $6.2 \times 10^{-4} \text{ m}$

30.22: Nichrome

▣ Office hours...

MW 10-11 am

TR 9-10 am

F 12-1 pm

▣ Tutorial Learning Center (TLC) hours:

MTWR 8-6 pm

F 8-11 am, 2-5 pm

Su 1-5 pm

Chapter 31

Fundamentals of Circuits *(Kirchoff's Laws and the Basic Circuit & Energy and Power)*

Review...

- ▣ *Kirchoff's junction rule..*

$$\sum I_{in} = \sum I_{out}$$

- ▣ *Kirchoff's loop rule...*


$$\sum (\Delta V)_i = 0$$

i.e. 31.1:

Two resistors and two batteries


Analyze the circuit shown in the figure.

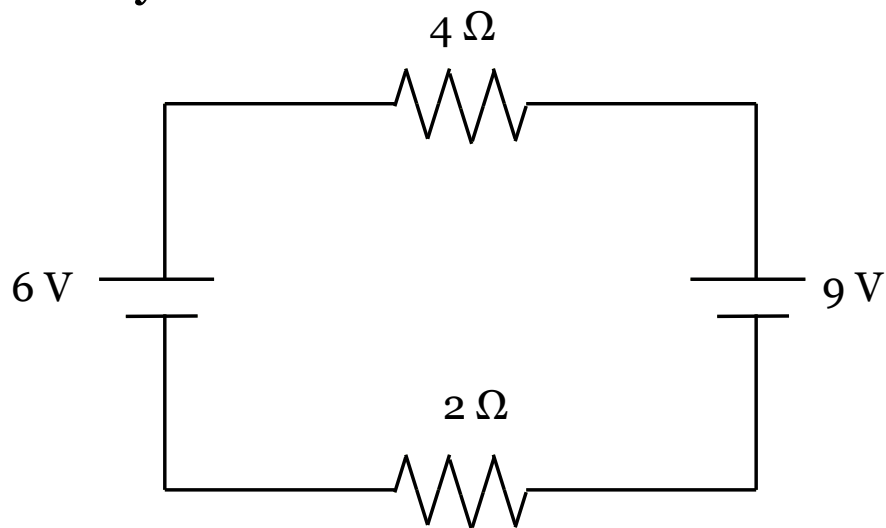- Find the current in and the potential difference across each resistor.
- Draw a graph showing how the potential changes around the circuit, starting from $V = 0\text{V}$ at the negative terminal of the 6V battery.





The Basic Circuit

Consider the basic circuit shown...

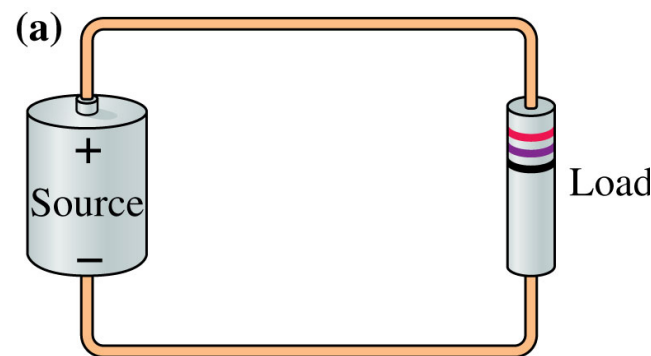

The Basic Circuit

Consider the basic circuit shown...

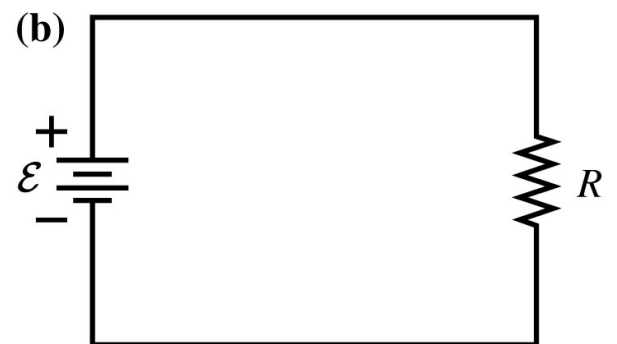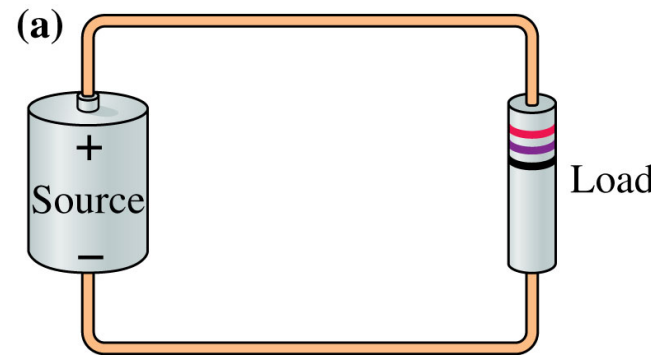


Notice:

1. NO junctions, SAME I everywhere.
2. Assuming ideal wires ($R_{\text{wire}} \sim 0$).

Quiz Question 1


The potential difference across the $10\ \Omega$ resistor is...

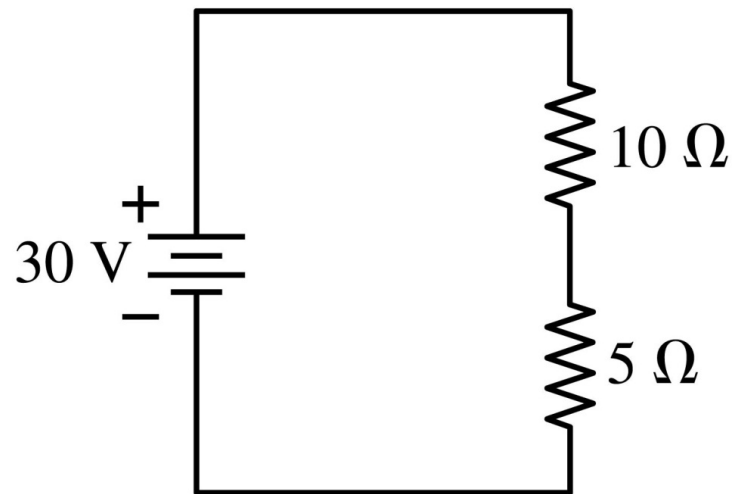1. 30 V.
2. 20 V.
3. 15 V.
4. 10 V.
5. 5 V.



Quiz Question 2

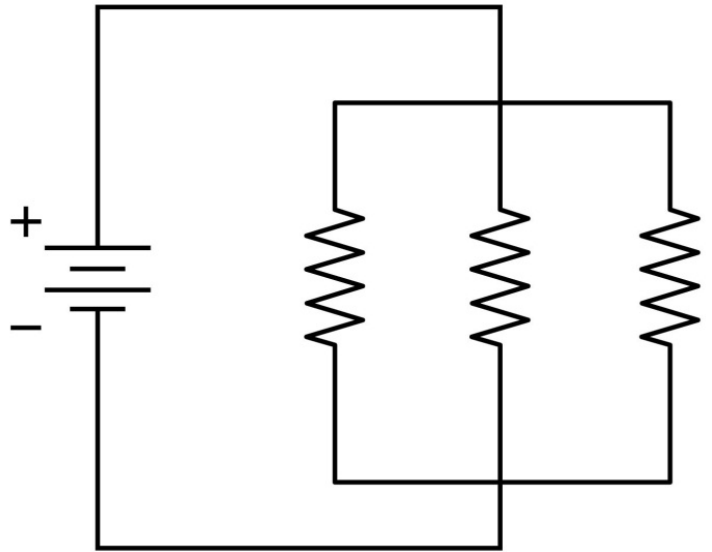
What things about the resistors in this circuit are the same for all three?



1. Current, I .
2. Potential difference, ΔV .
3. Resistance, R .
4. 1. and 2.
5. 2. and 3.

Quiz Question 3


Which light bulb is brighter?

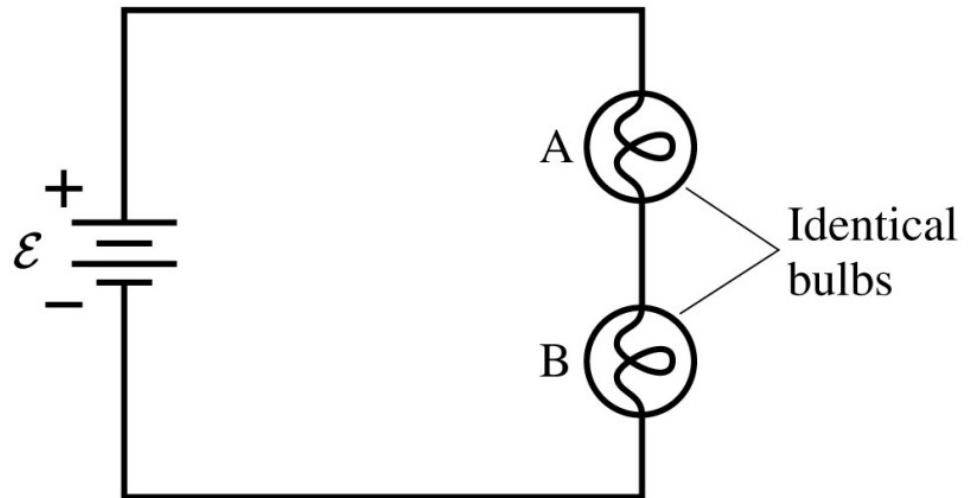

1. Light bulb A.
2. Light bulb B.
3. Both are the same brightness.

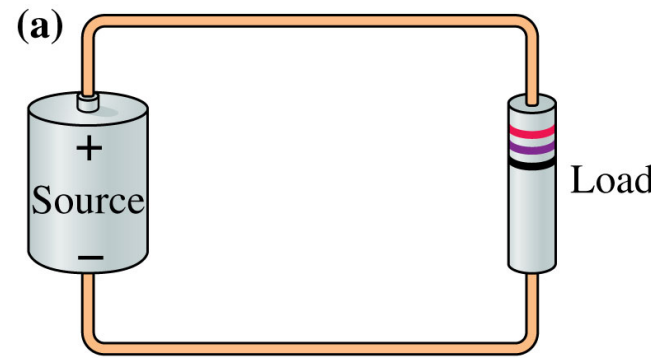31.3: Energy and Power


Current is NOT used up by the light bulb, ENERGY is!



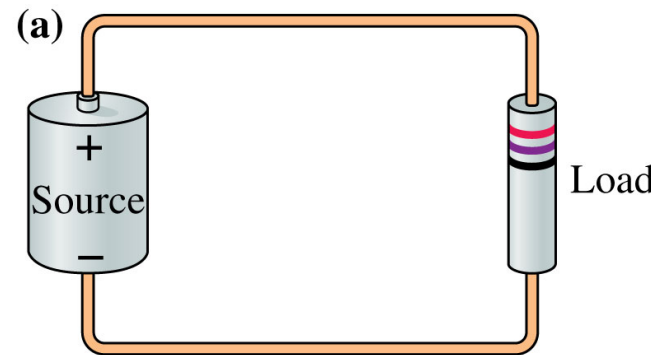31.3: Energy and Power

Current is NOT used up by the light bulb, ENERGY is!

Q: What is the rate at which the battery supplies energy to the charges?



31.3: Energy and Power


Current is NOT used up by the light bulb, ENERGY is!

Q: What is the rate at which the battery supplies energy to the charges?

A:

$$P_{bat} = I\mathcal{E}$$

SI Units?

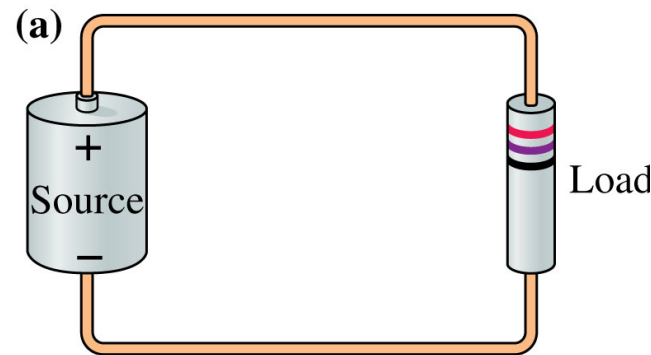

31.3: Energy and Power

Current is NOT used up by the light bulb, ENERGY is!


Q: What is the rate at which the battery supplies energy to the charges?

A:

$$P_{bat} = I\mathcal{E}$$

SI Units?

$$[P] = \text{J/s or W}$$

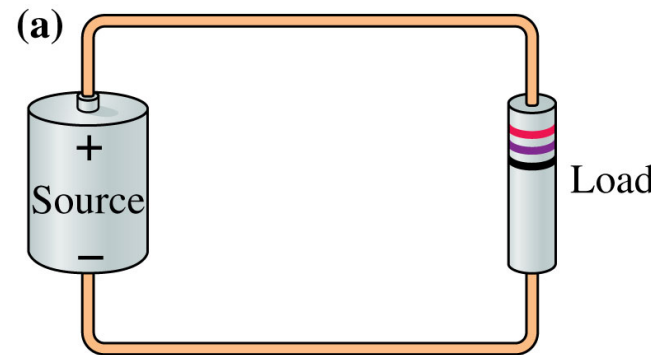

i.e. 31.2:

Delivering Power

A $90\ \Omega$ load is connected to a 120V battery.

How much power is delivered by the battery?

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

Q: Where does that energy go?

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

Q: Where does that energy go?

A: $E_{\text{chem}} \rightarrow U \rightarrow K \rightarrow E_{\text{th}}$

- ▣ The battery's *chemical energy* is transferred to the *thermal energy* of the resistors.
- ▣ The *rate* at which the battery supplies energy is *exactly equal to* the *rate* at which the resistor dissipates energy!

i.e. 31.3:

The power of light

How much current is “drawn” by a 100 W light bulb connected to a 120 V outlet?

What’s the resistance of the light bulb?

31.3: Energy and Power

Power dissipated by a resistor..

31.3: Energy and Power

Power dissipated by a resistor..

$$P_R = I \Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$


Notice:

For resistors in *series*, the resistor with the *largest* resistance dissipates the *most* power.

For resistors in *parallel*, the resistor with the *smallest* resistance dissipates the *most* power.

Quiz Question 4

Which resistor dissipates more power?

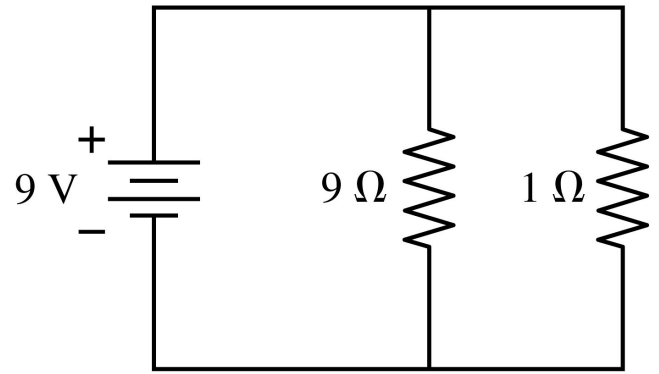

1. The $9\ \Omega$ resistor.
2. The $1\ \Omega$ resistor.
3. They dissipate the same power.