

Problem 2.1

Collector Emitter Circuit

$$3.3V - 2V - 330 I - 0.6 = 0$$

↑
LED diode

↑
BE diode

$$0.7 = 330 I$$

$$I \approx 2 \text{ mA}$$

Base - Emitter


$$3.3V - I \cdot 10000 - 0.6V = 0$$

$$10000 I = 2.7V$$


$$I \approx 0.3 \text{ mA}$$

$$\beta \geq 10!$$

so typically in saturation

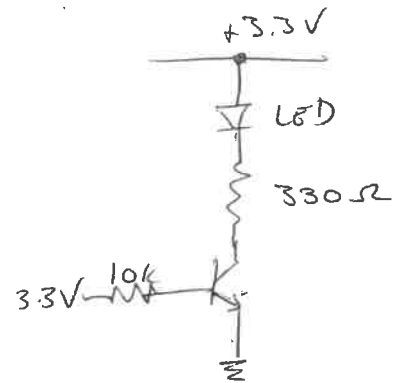

Problem 2.4

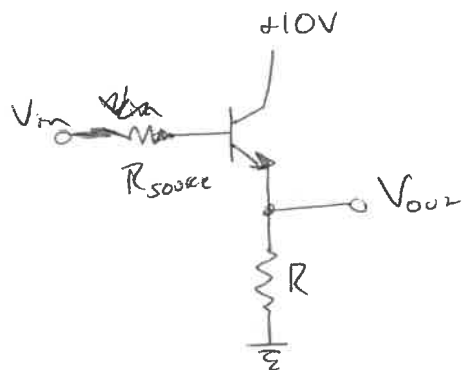

Make a small change ΔV_B at emitter.

$$\Delta I_B = \frac{\Delta V_B}{R_S} = \frac{\Delta V_E}{R_S}$$

still have $I_E = I_C + I_B$

$$I_E = (\beta + 1) I_B$$

$$\Delta I_B = \frac{\Delta I_E}{\beta + 1}$$

$$\frac{\Delta I_E}{\beta + 1} = \frac{\Delta V_E}{R_S}$$


$$V = I R$$

$$R = \frac{V}{I}$$

$$\frac{R_S}{\beta + 1} = \frac{\Delta V_E}{\Delta I_E} = r_{out}$$

$$r_{out} = \frac{Z_{source}}{\beta + 1}$$

Problem 2.5

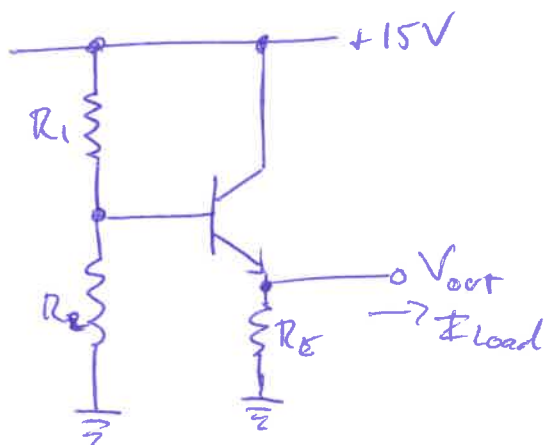

$$\text{max } I_{\text{Load}} = 25 \text{ mA}$$

$$\text{pick } R_E = 1 \text{ k}$$


$$\text{want } V_{\text{out}} = 5 \text{ V so current through } R_E, I_E \approx \frac{5 \text{ V}}{1000 \Omega} = 5 \text{ mA}$$

$$\text{so total current at emitter node under full load is } 25 \text{ mA} + 5 \text{ mA} = 30 \text{ mA}$$

$$\text{So base current under load} \approx \frac{30 \text{ mA}}{\beta}$$

$$I_B = 3 \times 10^{-4} \text{ A at } \beta = 100.$$

So now look at divider,

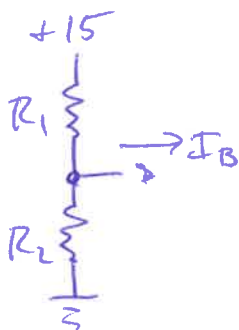

with no load, $I_B = 0$ want V across R_2 to be 5.6 V , ~~so~~ (lose $\sim 0.6 \text{ V}$ across transistor)


$$5.6 \text{ V} = \frac{R_2}{R_1 + R_2} 15 \text{ V}$$

$$5.6 R_1 + 5.6 R_2 = 15 R_2$$

$$5.6 R_1 = 9.4 R_2$$

$$R_2 = \frac{5.6}{9.4} R_1$$

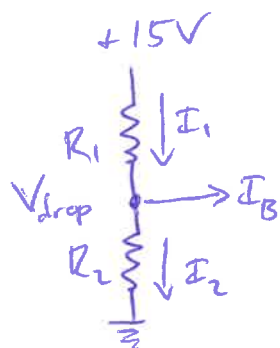with our I_B load, we don't want voltage to drop by more than 5%



$$V_{\text{drop}} = 5.6 \text{ V} - 0.05(5.6 \text{ V}) = 0.95(5.6 \text{ V})$$

$$I_1 = I_2 + I_B$$

$$\frac{V_1}{R_1} = \frac{V_2}{R_2} + I_B$$

$$V_1 = 15 - (0.95)(5.6)$$

$$V_2 = 0.95(5.6)$$

$$\frac{15 - 0.95(5.6)}{R_1} = \frac{0.95(5.6)}{R_2} + I_B$$

plug in R_2 from above.

$$\frac{15}{R_1} - \frac{0.95(5.6)}{R_1} = \frac{0.95(5.6)}{5.6 R_1} + I_B$$

$$\frac{15}{R_1} - (0.95) \frac{15}{R_1} = I_B$$

$$\frac{0.05(15)}{R_1} = I_B$$

$$R_1 = \frac{(0.05)(15)}{I_B} = 2500 \Omega$$

$$\text{so } R_2 = 1440 \Omega$$