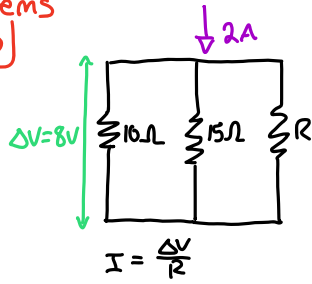


Problems
31. P. 20



$$I_{in} = I_{out}$$

$$I = \frac{\Delta V}{R}$$

$$I_1: \Delta V = 8V$$

$$R_1 = 10\Omega$$

$$I_2: \Delta V = 8V$$

$$R = 15\Omega$$

$$I_3 = ?$$

$$I_3: R = \frac{\Delta V}{I_3}$$

$$\Delta V = 8V$$

$$I_3 = 0.67A$$

$$R = 12\Omega$$

$$I_1 = 0.8A$$

$$I_2 = 0.53A$$

$$2A_{in} = 2A_{out}$$


$$I_1 + I_2 + I_3 = I_T$$

$$I_3 = 2A - 0.8A - 0.53A$$

$$I_3 = 0.67A$$

$$R_3 = 12\Omega$$

31. P. 22

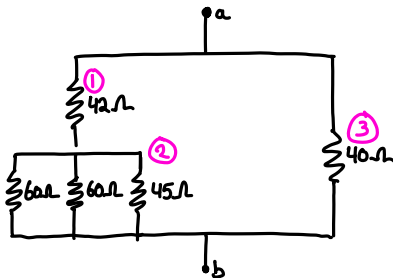

Parallel: Add like capacitors in series

Series: Add like capacitors in parallel

$$2: \frac{1}{R_{eq}} = \left(\frac{1}{60\Omega} + \frac{1}{60\Omega} + \frac{1}{45\Omega} \right)$$

$$R_{eq} = 18\Omega$$

$$R_A = R_1 + R_2: 42\Omega + 18\Omega = 60\Omega$$

$$R_A + R_3: \frac{1}{R_{eq}} = \left(\frac{1}{60\Omega} + \frac{1}{40\Omega} \right)$$


$$R_{eq} = 24\Omega$$

Between A & B

$$R = 24\Omega$$

$$24\Omega$$

31. P. 46

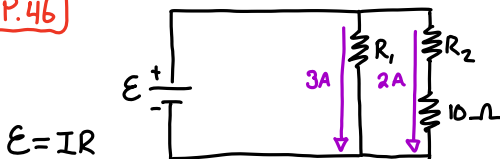

$$E = IR$$

$$E = 60V$$

$$1: I = \frac{\Delta V}{R} \quad \Delta V = E$$

$$R = \frac{\Delta V}{I_1} \quad I_1 = 3A$$

$$I_2 = 2A \quad \Delta V = E = \frac{2A(10\Omega)}{(1 - \frac{2A}{3A})} = \frac{20A\Omega}{\frac{1}{3}}$$

$$E = 60V$$

$$2: R_{eq} = 10\Omega + R \quad \Delta V = IR_{eq}$$

$$\frac{\Delta V}{I_2} = 10\Omega + \frac{\Delta V}{I_1}$$

$$\Delta V = I_2(10\Omega + \frac{\Delta V}{I_1})$$

$$\Delta V = I_2 10\Omega + \frac{I_2 \Delta V}{I_1}$$

$$\Delta V - \frac{I_2 \Delta V}{I_1} = I_2 10\Omega$$

$$\Delta V(1 - \frac{I_2}{I_1}) = I_2 10\Omega$$

$$\Delta V = \frac{I_2 10\Omega}{(1 - \frac{I_2}{I_1})}$$

$$I = \frac{\Delta V}{R} : \Delta V = IR$$

$$R_{eq} < R_A$$

Conceptual
31. C. 10

a.) Since B & C have the same resistance and current, their scenario is equivalent to each other

$$A > B = C$$

b.) When a wire is added between 1 & 2, the current through B & C disappears due to the wire having no resistance. Current flow B and C is zero. This then means the resistance is smaller and thus A would be brighter.

B & C go out
A Brightens