

# Announcements

---

## ▣ Homework for tomorrow...

Ch. 30: CQ 11, Probs. 28, 34, & 58

CQ6:  $I_a = I_d > I_b = I_c$

30.10: a)  $J = 1.7 \times 10^7 \text{ A/m}^2$     b)  $i_e = 5.3 \times 10^{18} \text{ s}^{-1}$

30.14:  $D = 1.8 \times 10^{-3} \text{ m}$

30.16:  $J = 42. \times 10^6 \text{ A/m}^2$

## ▣ Office hours...

MW 10-11 am

TR 9-10 am

F 12-1 pm

## ▣ Tutorial Learning Center (TLC) hours:

MTWR 8-6 pm

F 8-11 am, 2-5 pm

Su 1-5 pm

# Chapter 30

---

## Current & Resistance (*Resistance and Ohm's Law*)

# Review...

---

- *Current density related to the  $E$ -field...*

$$J = \sigma E$$

- *Resistivity & conductivity...*

$$\rho = \frac{1}{\sigma} = \frac{m}{n_e e^2 \tau}$$

- *Ohm's Law...*

$$I = \frac{\Delta V}{R}$$

where

$$R = \frac{\rho L}{A}$$

## Quiz Question 1

Wire 2 has *twice* the length and *twice* the diameter of wire 1. What is the ratio  $R_2/R_1$  of their resistances?

$$L_2 = 2L_1$$


$$A_2 = 4A_1$$

$$R_2 = \frac{\rho L_2}{A_2}$$

$$R_1 = \frac{\rho 2L_1}{4A_1}$$

$$R_1 = \frac{\rho L_1}{A_1}$$


1. 1/4.
- ② 1/2.
3. 1.
4. 2.
5. 4.

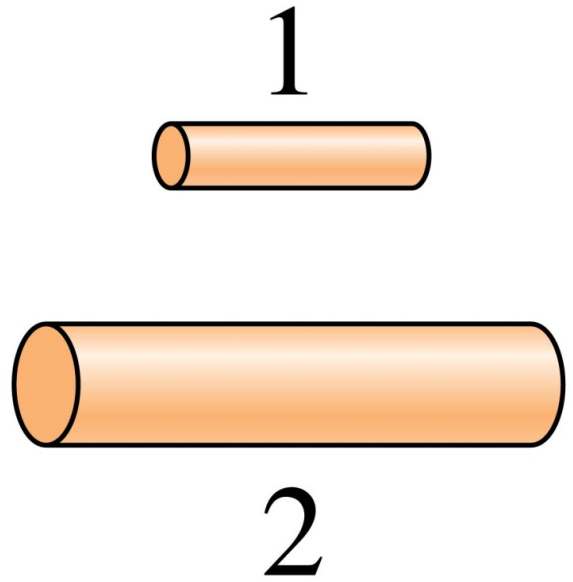

# Resistance and Ohm's Law

- A battery is a *source* of potential difference  $\Delta V_{\text{bat}}$ .
- The battery *creates* a potential difference  $\Delta V_{\text{wire}} = \Delta V_{\text{bat}}$  between the ends of the wire.
- The potential difference in the wire  $\Delta V_{\text{wire}}$  generates an  $E$ -field in the wire.
- The  $E$ -field establishes a current  $I = JA = \sigma AE$  in the wire.
- The current in the wire is determined *jointly* by the battery and the wire's resistance,  $R$  to be:

$$\square I = \Delta V_{\text{wire}}/R$$

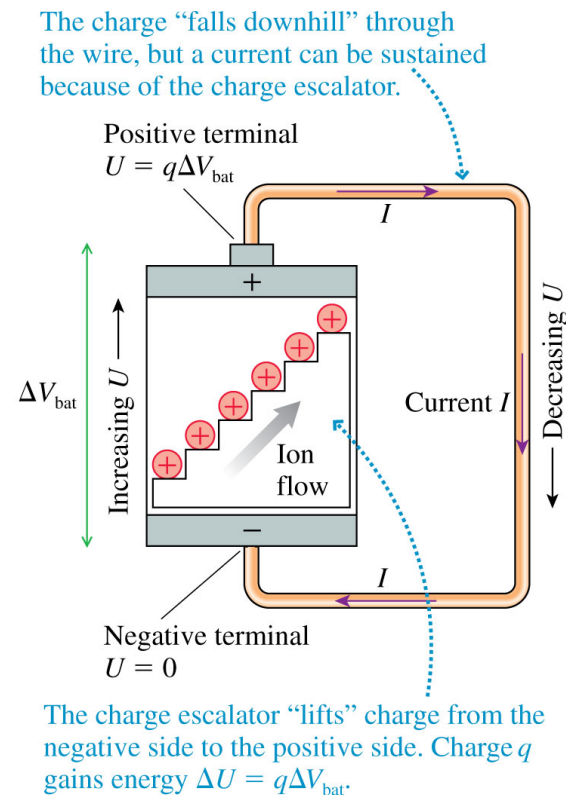


# Resistance and Ohm's Law

---

Notice: Ohm's Law is NOT a Law!

The materials to which Ohm's law applies are called *Ohmic*.

□ i.e.'s: metals and conductors

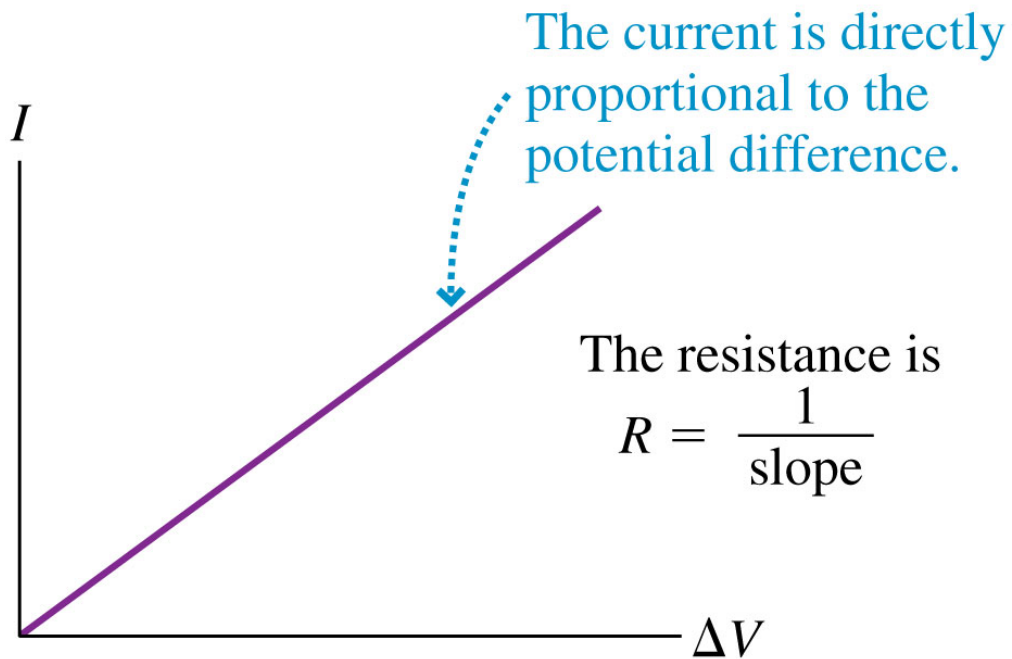


# Resistance and Ohm's Law

---

*Nonohmic materials:*

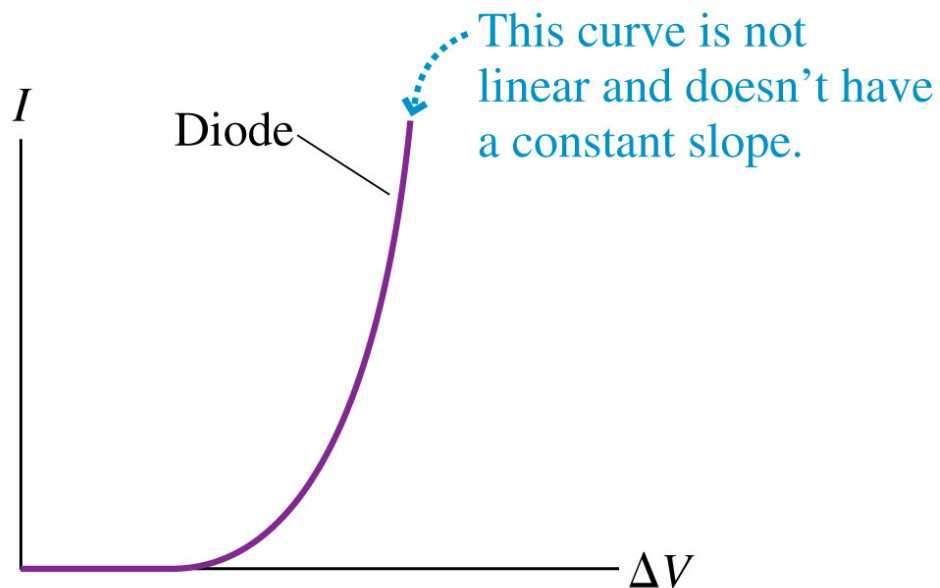
- *current,  $I$* , through the device is *NOT* directly proportional to the *potential difference,  $\Delta V$* .
- i.e.'s: diodes, batteries, and capacitors




## Quiz Question 2

The current through a wire is measured as the potential difference  $\Delta V$  is varied.

What is the wire's resistance?

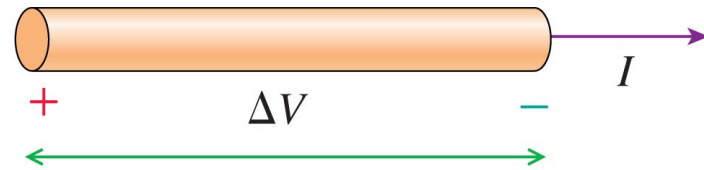

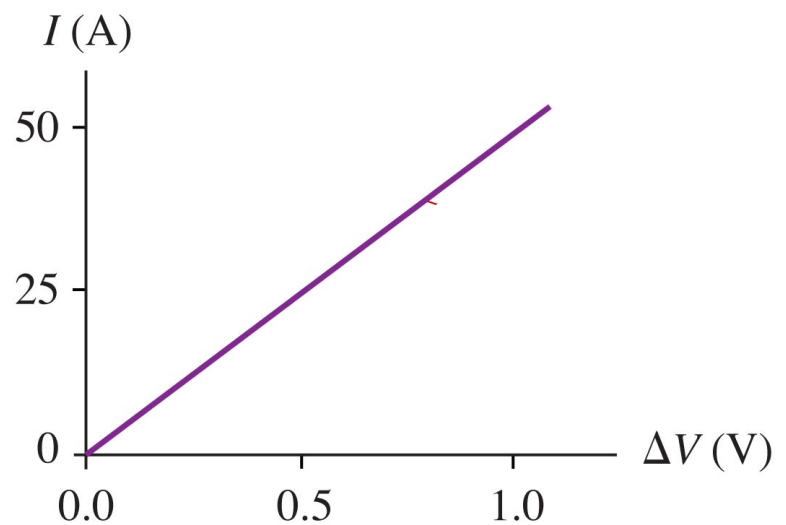
1. 0.01  $\Omega$ .
- ② 0.02  $\Omega$ .
3. 50  $\Omega$ .
4. 100  $\Omega$ .
5. Some other value.




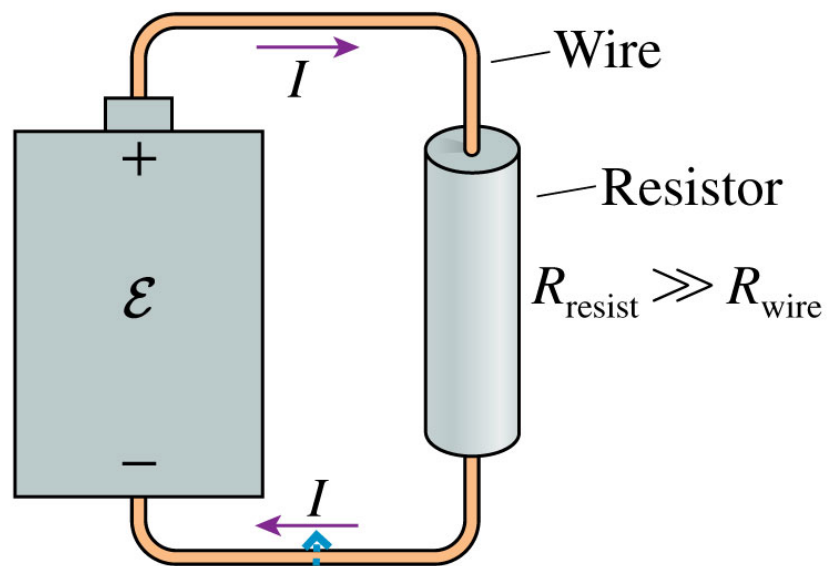
# Resistance and Ohm's Law

Q: How does the voltage drop across the wires compare to the voltage drop across the resistor?




The current is constant along the wire-resistor-wire combination.
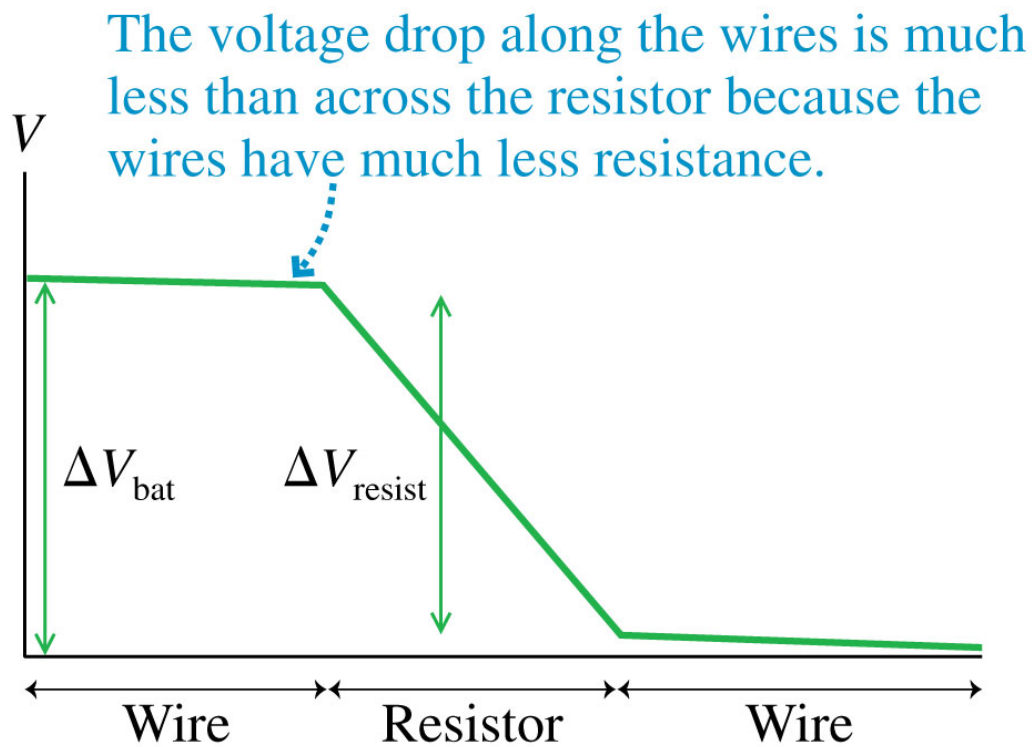
# Resistance and Ohm's Law

Q: How does the voltage drop across the wires compare to the voltage drop across the resistor?

A:  $\Delta V_{\text{wire}} \ll \Delta V_{\text{resist}}$



i.e. 30.8:

## A battery and a resistor

---

What resistor would have a 15 mA current if connected across the terminals of a 9.0 V battery?

$$I = \frac{\Delta V}{R} \quad \begin{array}{l} \Delta V = 9.0 \text{ V} \\ I = 15 \times 10^{-3} \text{ A} \end{array}$$

$$R = \frac{\Delta V}{I}$$

$$R = 600 \, \Omega$$