

Name: Taylor Carrenea

$$X_c = \frac{1}{\omega C}$$


Electronics for Scientists

RC Highpass Filter

Instructions

Complete the following exercises to the best of your ability.

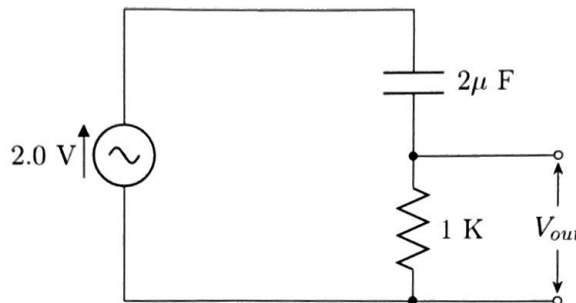- Determine the reactance of a capacitor with a capacitance equal to $0.5 \mu\text{F}$ at frequencies of 10 Hz, 100 kHz, and 10 MHz.
- The circuit shown below has a 2.0 V AC signal in series with a $0.5 \mu\text{F}$ capacitor and a 1 K resistor. Treat the circuit as a voltage divider to find the output voltage at frequencies 10 Hz, 1 kHz, 100 kHz, and 10 MHz.



$$\omega = 2\pi f$$

$$X_c = \frac{1}{\omega C}$$

- The above circuit is a highpass filter. What is its 3 dB frequency?

1. $f = 10 \text{ Hz}$: $X_c = \frac{1}{2\pi(10 \text{ Hz})(0.5 \times 10^{-6} \text{ F})} = 31,831 \Omega$

$$X_{10} = 31,831 \Omega$$

$$V_{out} = \left(\frac{\omega R C}{1 + \omega R C} \right) V_{in}$$

$f = 100 \text{ kHz}$: $X_c = \frac{1}{2\pi(100 \text{ kHz})(0.5 \times 10^{-6} \text{ F})} = 3.1831 \Omega$

$$X_{100} = 3.18 \Omega$$

$$V_o = \left(\frac{\omega R C}{\sqrt{1 + (\omega R C)^2}} \right) V_{in}$$

$f = 10 \text{ MHz}$: $X_c = \frac{1}{2\pi(10 \text{ MHz})(0.5 \times 10^{-6} \text{ F})} = 0.031831 \Omega$

$$f_{3dB} = \frac{1}{2\pi R C}$$

$$X_{10} = 0.0318 \Omega$$

2. V_{out} : $f = 10 \text{ Hz}$: $V_o = \left(\frac{2\pi(10 \text{ Hz}) \cdot R C}{\sqrt{1 + (2\pi(10 \text{ Hz}) \cdot R C)^2}} \right) V_{in} = 0.249 \text{ V}$

$$V_{10 \text{ Hz}} = 0.249 \text{ V}$$

$R = 1 \text{ K}\Omega$
 $C = 2 \mu\text{F}$
 $V_{in} = 2 \text{ V}$

$f = 1 \text{ kHz}$: $V_o = \left(\frac{2\pi(1 \text{ kHz}) \cdot R C}{\sqrt{1 + (2\pi(1 \text{ kHz}) \cdot R C)^2}} \right) V_{in} = 1.99 \text{ V}$

$$V_{1 \text{ kHz}} = 1.99 \text{ V}$$

$f = 100 \text{ kHz}$: $V_o = \left(\frac{2\pi(100 \text{ kHz}) \cdot R C}{\sqrt{1 + (2\pi(100 \text{ kHz}) \cdot R C)^2}} \right) V_{in} = 2 \text{ V}$

$$V_{100 \text{ kHz}} = 2 \text{ V}$$

$f = 10 \text{ MHz}$: $V_o = \left(\frac{2\pi(10 \text{ MHz}) \cdot R C}{\sqrt{1 + (2\pi(10 \text{ MHz}) \cdot R C)^2}} \right) V_{in} = 2 \text{ V}$

$$V_{10 \text{ MHz}} = 2 \text{ V}$$

3. $f_{3dB} = \frac{1}{2\pi R C} = \frac{1}{2\pi(1 \text{ K}\Omega)(2 \mu\text{F})} = 79.5 \text{ Hz}$

$R = 1 \text{ K}\Omega$
 $C = 2 \mu\text{F}$

$$f_{3dB} = 79.5 \text{ Hz}$$

Taylor Larrabee

Dr. Henderson PHS 201 HW

September 12, 2017

HW 4

1.33 RC low pass attenuates to 6 dB?
Phase shift?

$$\begin{aligned} \text{a.) } V_1 &= \frac{1}{2} V_0 & \text{dB} &= 20 \log_{10} \left(\frac{V_1}{V_0} \right) & \frac{V_1}{V_0} &= \frac{1}{2} \\ & & &= 20 \log_{10} \left(\frac{1}{2} \right) & & \\ & & \text{dB} &= -6.02 \text{ dB} & & \end{aligned}$$

b.) The phase shift of this would be 0° .

$$\frac{V_1}{V_0} = (1 + \omega^2 R^2 C^2)^{-\frac{1}{2}}$$

$$\left(\frac{V_1}{V_0} \right)^2 = 1 + \omega^2 R^2 C^2$$

$$4 - 1 = \omega^2 R^2 C^2$$

$$\frac{3}{R^2 C^2} = \omega^2$$

$$\frac{\sqrt{3}}{RC} = \omega$$

$$f = \frac{1}{\omega RC} = \frac{1}{\sqrt{3} \frac{\sqrt{3}}{RC}} = \frac{1}{3} = 0.33 \text{ Hz}$$

$$f = 0.57 \text{ Hz}$$