
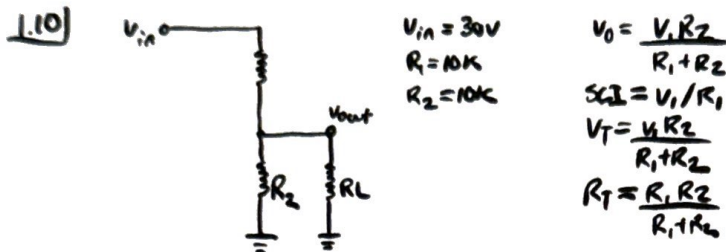


3/3

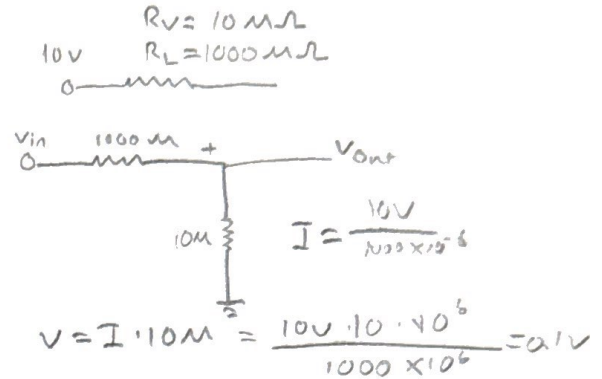1.9] Since you can connect the resistor in series with the voltmeter, you create a ^{smaller} ~~smaller~~ ^{bigger} resistance in the circuit thus making a ~~smaller~~ ^{bigger} current. If you wanted to measure the leakage resistance all you'd have to do is use $V = IR$.




a.) $V_0?$ $V_i = 30\text{V}$
 $R_1 = 10\text{K}$
 $R_2 = 10\text{K}$


$V_0 = \frac{30\text{V}(10\text{K})}{20\text{K}} = \frac{300}{20} = 15\text{V}$

$V_0 = 15\text{V}$


b.) 10K load

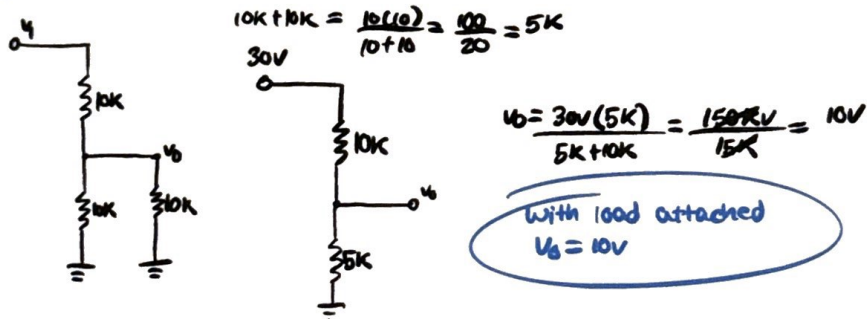

c.) Thevenin

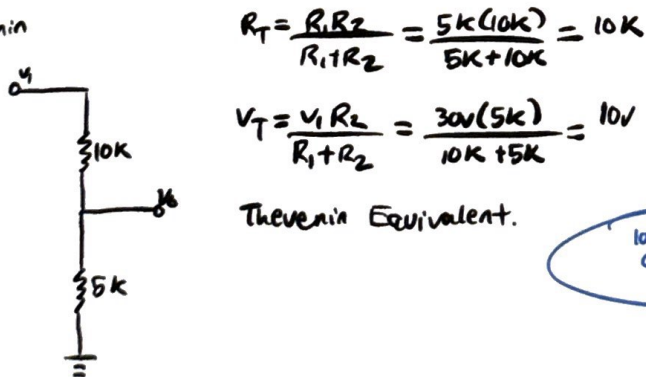


d.)

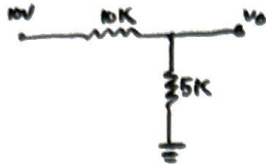

$$V_o = \frac{4(R_2)}{R_1 + R_2} = \frac{10V(5K)}{10K + 5K} = \frac{150KV}{15K} = 10V$$

$$V_o = 10V$$

e.)

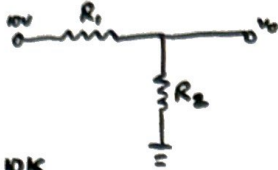

$$P? \quad P = R \cdot I^2$$

$$P_1: P = 10KA(1A)^2 = 10W$$

$$P_2: P = 5KA(1A)^2 = 5W$$


$$\begin{aligned} R_1 &= 10K \\ R_2 &= 5K \\ I &= 1A \end{aligned}$$

$$P_1 = 10W$$

$$P_2 = 5W$$

1.11

Proposed Circuit

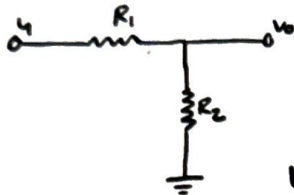

$$R_1 = R_2: \frac{2(2)}{2+2} = \frac{4}{4} = 1$$


$$R_1 \neq R_2: \frac{2(1)}{2+1} = \frac{2}{3} = \frac{2}{3}$$

$$P = V^2/R, \quad P = IV, \quad P = I^2R$$

$$V = \frac{10V(5K)}{5K + 20K} = 2K \quad V = \frac{10V(5K)}{5K + 5K} = 5K$$

when $R_L = R_S$, there is a higher output voltage indicating the power will be greater due to the resistances being the same with a greater voltage.

$$P = V^2/R$$

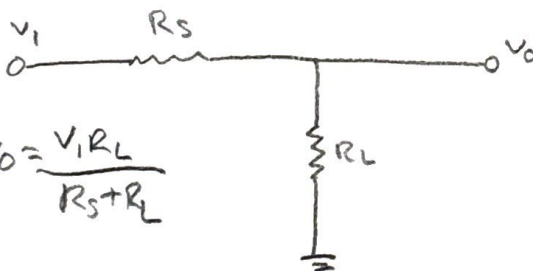

$$P = \frac{V_o^2}{R_L}$$

$$V_o = \frac{V_1 R_L}{R_S + R_L}$$

$$P = \frac{V_1^2 R_L^2}{R_L (R_S + R_L)^2}$$

$$\frac{dP}{dR_L} \rightarrow \text{set} = 0$$