

Announcements

▣ Homework for tomorrow...

Ch. 31: CQ 3, Probs. 1, 6, & 8

CQ10: a) doubles b) unchanged c) unchanged d) doubles

30.18: $\tau_{Al} = 2.1 \times 10^{-14} \text{ s}$, $\tau_{Fe} = 4.3 \times 10^{-15} \text{ s}$

30.20: a) 10 V/m b) $6.7 \times 10^6 \text{ A/m}^2$ c) $6.2 \times 10^{-4} \text{ m}$

30.22: Nichrome

▣ Office hours...

MW 10-11 am

TR 9-10 am

F 12-1 pm

▣ Tutorial Learning Center (TLC) hours:

MTWR 8-6 pm

F 8-11 am, 2-5 pm

Su 1-5 pm

Chapter 31

Fundamentals of Circuits *(Kirchoff's Laws and the Basic Circuit & Energy and Power)*

Review...

- ▣ *Kirchoff's junction rule..*

$$\sum I_{in} = \sum I_{out}$$

- ▣ *Kirchoff's loop rule...*



$$\sum (\Delta V)_i = 0$$

i.e. 31.1:

Two resistors and two batteries



Analyze the circuit shown in the figure.

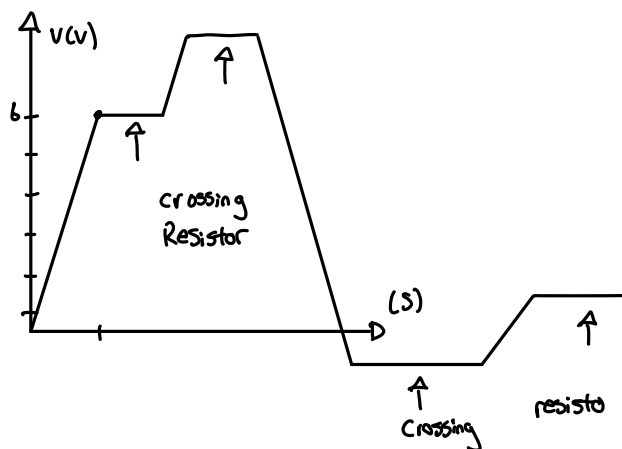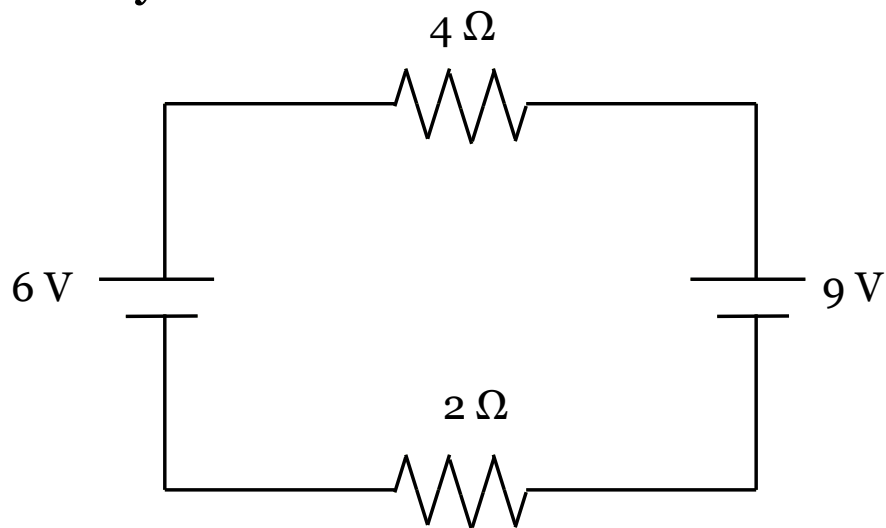- Find the current in and the potential difference across each resistor.
- Draw a graph showing how the potential changes around the circuit, starting from $V = 0\text{V}$ at the negative terminal of the 6V battery.





The Basic Circuit

Consider the basic circuit shown...

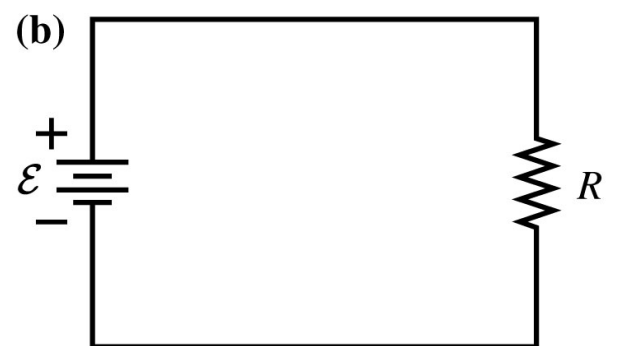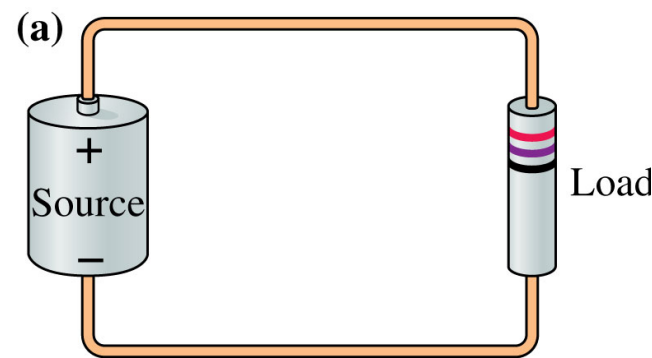

The Basic Circuit

Consider the basic circuit shown...

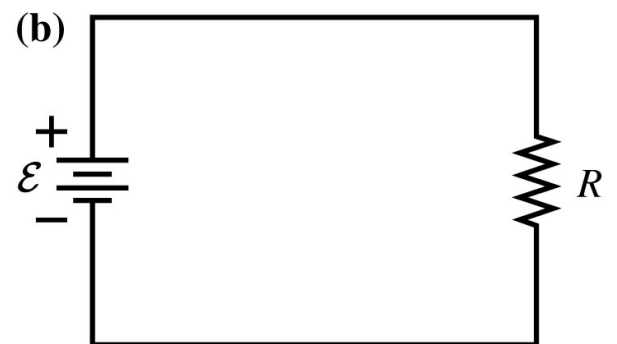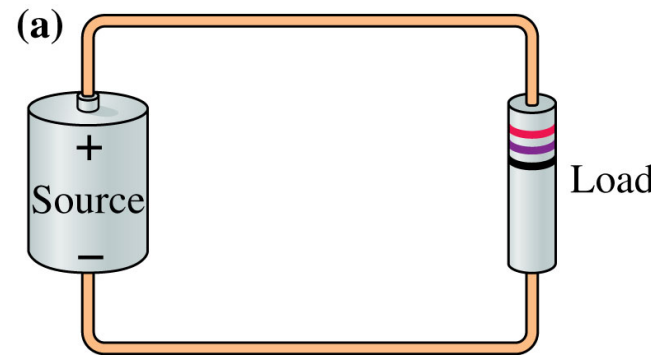


Notice:

1. NO junctions, SAME I everywhere.
2. Assuming ideal wires ($R_{\text{wire}} \sim 0$).

Quiz Question 1

The potential difference across the $10\ \Omega$ resistor is...

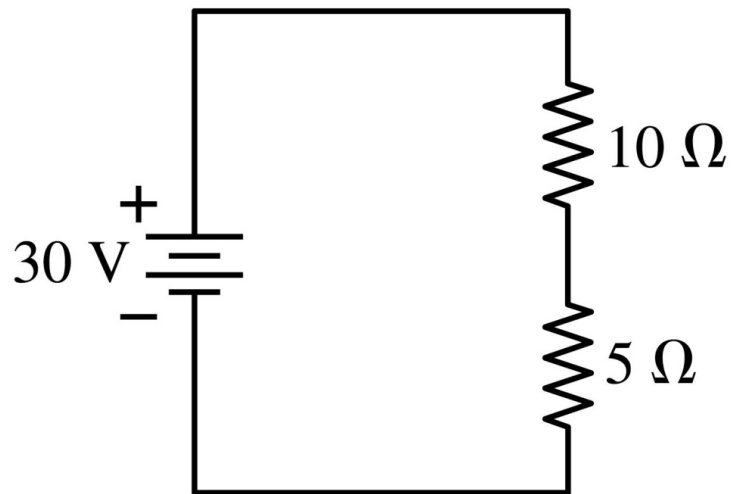
$$\begin{aligned} I &= \frac{\Delta V}{R} \\ \Delta V &= IR \\ 30\text{V} &= I(15\Omega) \\ I &= 2.0\text{A} \\ \Delta V &= 2.0\text{A}(10\Omega) \\ \Delta V &= 20\text{V} \end{aligned}$$



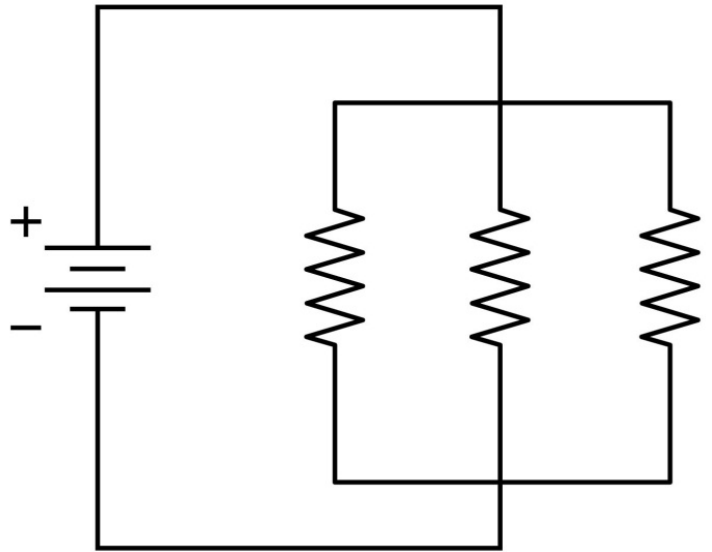1. 30 V.
2. 20 V.
3. 15 V.
4. 10 V.
5. 5 V.

Quiz Question 2


What things about the resistors in this circuit are the same for all three?



1. Current, I .
- ② Potential difference, ΔV .
3. Resistance, R .
4. 1. and 2.
5. 2. and 3.

Quiz Question 3


Which light bulb is brighter?

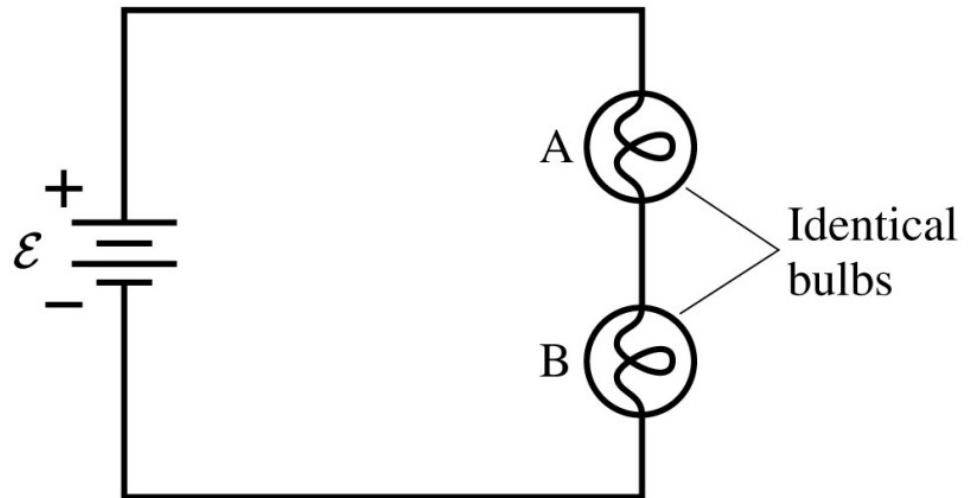

1. Light bulb A.
2. Light bulb B.
- ③ Both are the same brightness.

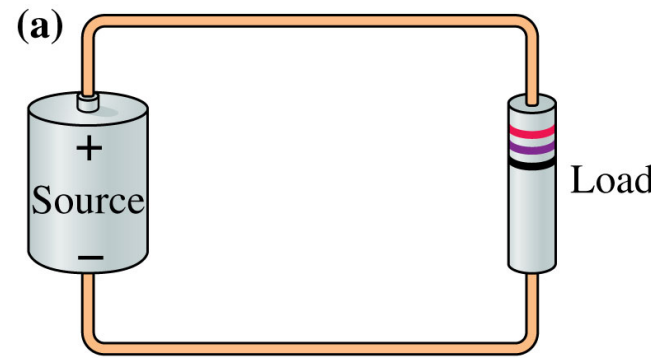31.3: Energy and Power

Current is NOT used up by the light bulb, ENERGY is!



31.3: Energy and Power

Current is NOT used up by the light bulb, ENERGY is!

Q: What is the rate at which the battery supplies energy to the charges?

A charge gains potential energy


$$\Delta U = q \Delta V = U - U_0$$

an ideal battery

$$\Delta V_{\text{Bat}} = \mathcal{E}_{\text{mf}}$$

$$U = q\mathcal{E}$$
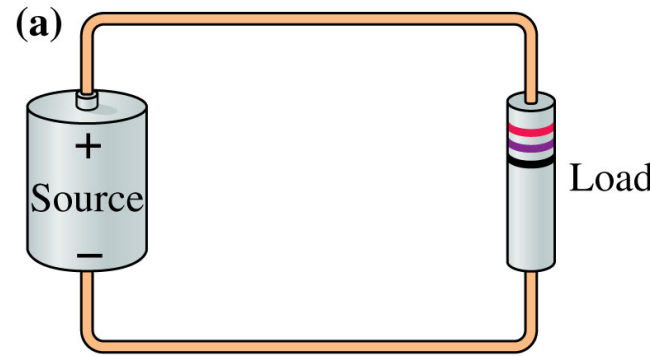
$$P_{\text{Bat}} = \frac{dU}{dt} = \frac{d}{dt}(q\mathcal{E}) = \mathcal{E} \frac{dq}{dt} \\ = I\mathcal{E}$$



31.3: Energy and Power


Current is NOT used up by the light bulb, ENERGY is!

Q: What is the rate at which the battery supplies energy to the charges?

A:

$$P_{bat} = I\mathcal{E}$$

SI Units?

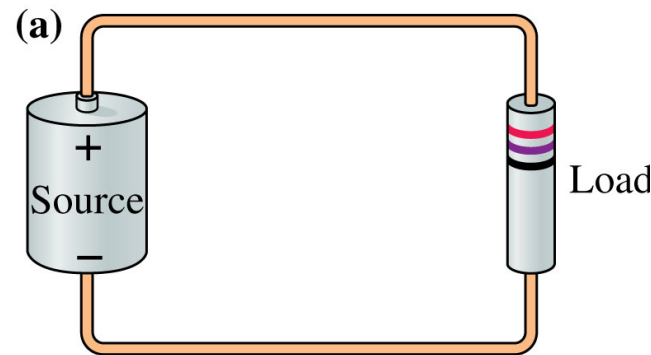

31.3: Energy and Power


Current is NOT used up by the light bulb, ENERGY is!

Q: What is the rate at which the battery supplies energy to the charges?

A: $P_{bat} = I\mathcal{E}$

SI Units?


$$[P] = \text{J/s or W}$$

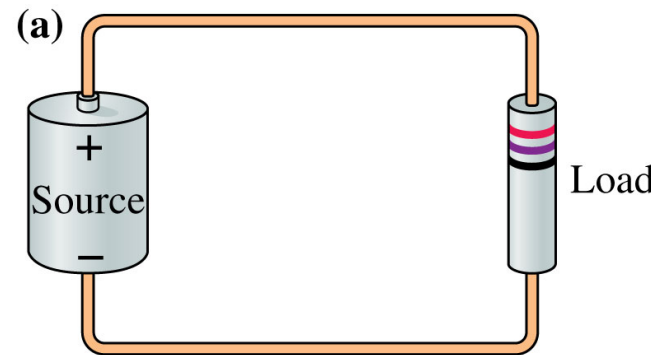

i.e. 31.2: Delivering Power

A $90\ \Omega$ load is connected to a 120V battery.

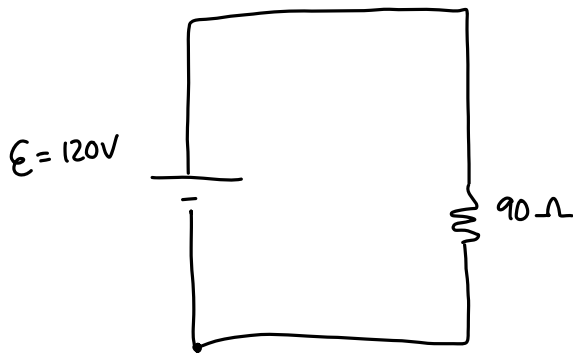How much power is delivered by the battery?



$$120\text{V} - I(90\ \Omega) = 0$$

$$I(90\ \Omega) = 120\text{V}$$

$$I = \frac{4}{3}\text{ A}$$

$$P_{\text{Bat}} = I\mathcal{E}$$

$$= \left(\frac{4}{3}\text{ A}\right)(120\text{V})$$

$$P_{\text{B}} = 160\text{ W}$$

$$P_{\text{B}} = 160\text{ W}$$

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

Q: Where does that energy go?

31.3:

Energy and Power

P_{bat} is the *energy transferred per second* from the battery's store of chemicals to the moving charges that make up the current.

Q: Where does that energy go?

A: $E_{\text{chem}} \rightarrow U \rightarrow K \rightarrow E_{\text{th}}$

- ▣ The battery's *chemical energy* is transferred to the *thermal energy* of the resistors.
- ▣ The *rate* at which the battery supplies energy is *exactly equal to* the *rate* at which the resistor dissipates energy!

i.e. 31.3:

The power of light

How much current is “drawn” by a 100 W light bulb connected to a 120 V outlet?

What's the resistance of the light bulb?

$$P_{\text{bat}} = I \mathcal{E}$$

$$\Delta V = I R$$

$$\mathcal{E} = 120\text{V}$$

$$P = I \mathcal{E}$$

$$R = \frac{\Delta V}{I}$$

$$I = \frac{P}{\mathcal{E}}$$

$$R = 144 \Omega$$

$$I = ?$$

$$P_{\text{bat}} = 100\text{W}$$

$$I = 0.83\text{A}$$

$$I = 0.83\text{A}$$

$$R = 144 \Omega$$

31.3: Energy and Power

Power dissipated by a resistor..

$$P_R = I \Delta V_R \quad I = \frac{\Delta V}{R}$$

$$P_R = \frac{\Delta V_R^2}{R} \quad \Delta V = IR$$

$$P_R = I^2 R$$

31.3: Energy and Power

Power dissipated by a resistor..

$$P_R = I \Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

Notice:


For resistors in *series*, the resistor with the *largest* resistance dissipates the *most* power.

For resistors in *parallel*, the resistor with the *smallest* resistance dissipates the *most* power.

Quiz Question 4

Which resistor dissipates more power?
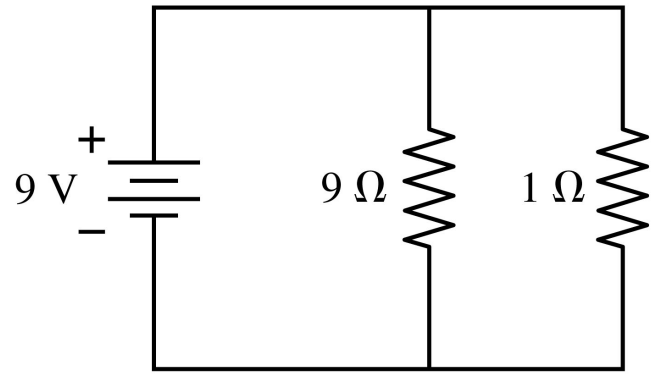
$$I = \frac{\Delta V}{R} \quad \Delta V = IR$$



1. The 9 Ω resistor.
2. The 1 Ω resistor.
3. They dissipate the same power.