

Name: Taylor Lurrechea

3


Electronics for Scientists

Diode Circuit


Instructions


Complete the following exercises to the best of your ability.

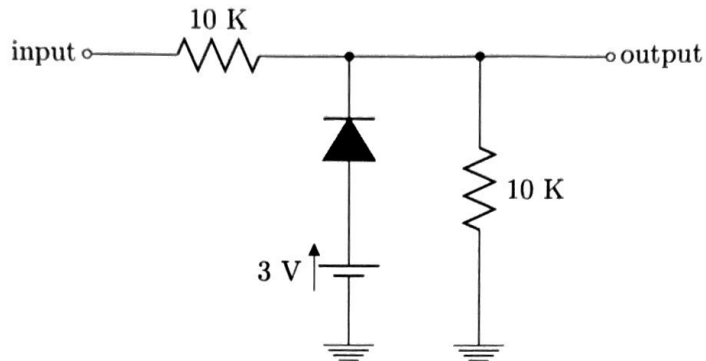1. A 60 Hz sinusoidal signal with a RMS voltage of 12 V is applied to the below circuit.



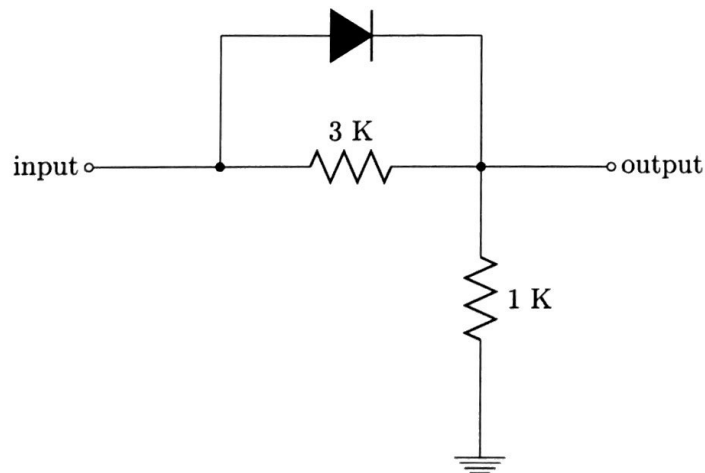
- If the diode is "off", what does the circuit look like?
 - If the diode is "on", what is the output voltage?
 - For what input voltage is the diode in the circuit "on"?
 - Sketch the output voltage versus time.
2. A 60 Hz sinusoidal signal with a RMS voltage of 12 V is applied to the below circuit. Sketch the output voltage versus time.



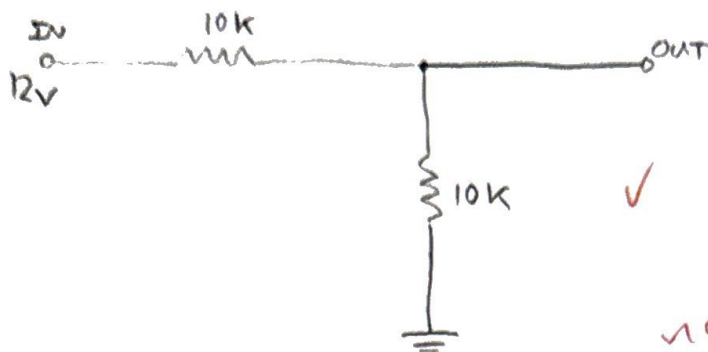

no resistors here
so it's a short!

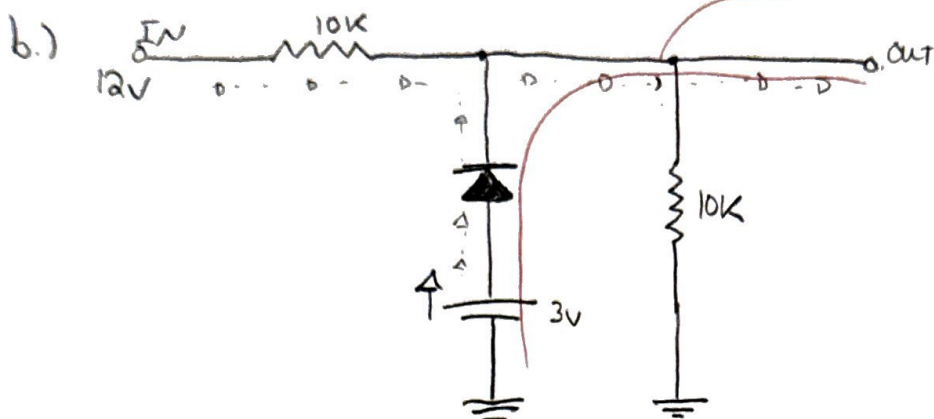$3V - 0.6V = V_{out}$
 $V_{out} = 2.4V$
 when diode on



$$12V - I(10k) - I(10k) = V_{out}$$

$$12.6V - I(10k) - 3.6V = V_{out}$$

$$V_{out} = 12V - (0.3mA)(10k) - 3.6V = 5.4V$$

$$12V - I(10k) - I(10k) = 9.0V - I(10k) - 3.6V$$


$$3.0V = I(10k)$$

$$I = \frac{3.0V}{10k} = 0.3mA$$


$$V_{out} = 5.4V$$

$$V = 12.6V$$

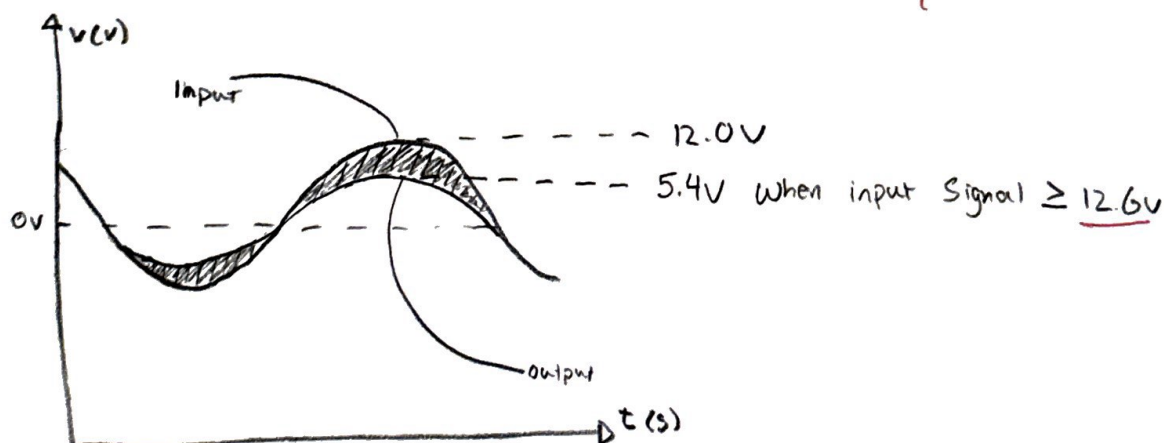c.) Since input is 12.0V, the required input voltage must be 12.6V to turn on the diode.



2) $f = 60 \text{ Hz}$

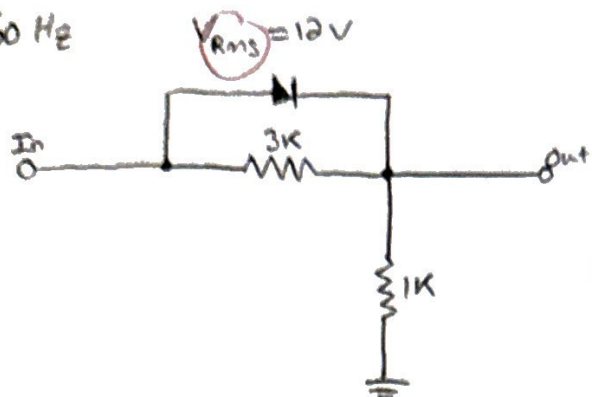

$V = 12\text{V}$

$$12\text{V} - I(3\text{k}) = V_{\text{out}}$$


$$12\text{V} - I(3\text{k}) - I(1\text{k}) = 0$$

$$I(4\text{k}) = 12\text{V}$$

$$I = \frac{12\text{V}}{4\text{k}} = 3\text{mA}$$


$$V_{\text{out}} = 12\text{V} - 3\text{mA}(3\text{k}) = 3\text{V}$$

$$V_{\text{out}} = 3\text{V}$$

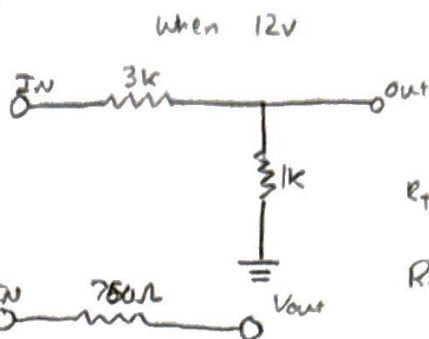

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{1(3)}{3+1} = \frac{3}{4}\text{k}$$

$$R_T = 750\Omega$$

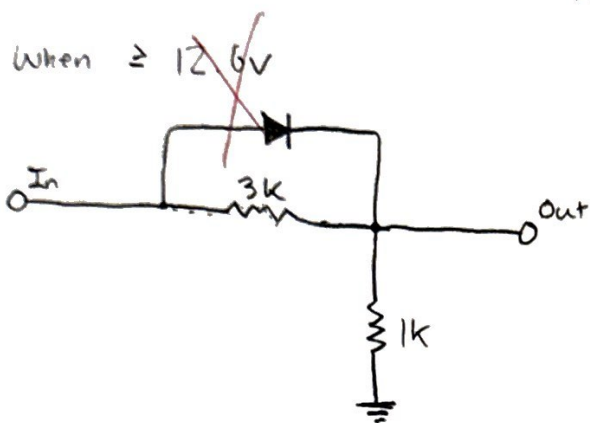

When $\geq 12.6\text{V}$

$$12.6\text{V} - I(3\text{k}) - 0.6\text{V} = V_{\text{out}}$$


$$12.6\text{V} - I(3\text{k}) - 0.6\text{V} - I(1\text{k}) = 0$$

$$12\text{V} = I(4\text{k})$$

$$I = 3\text{mA}$$


$$12\text{V} - 3\text{mA}(3\text{k}) - 0.6\text{V} = V_{\text{out}}$$

$$V_{\text{out}} = 2.4\text{V}$$

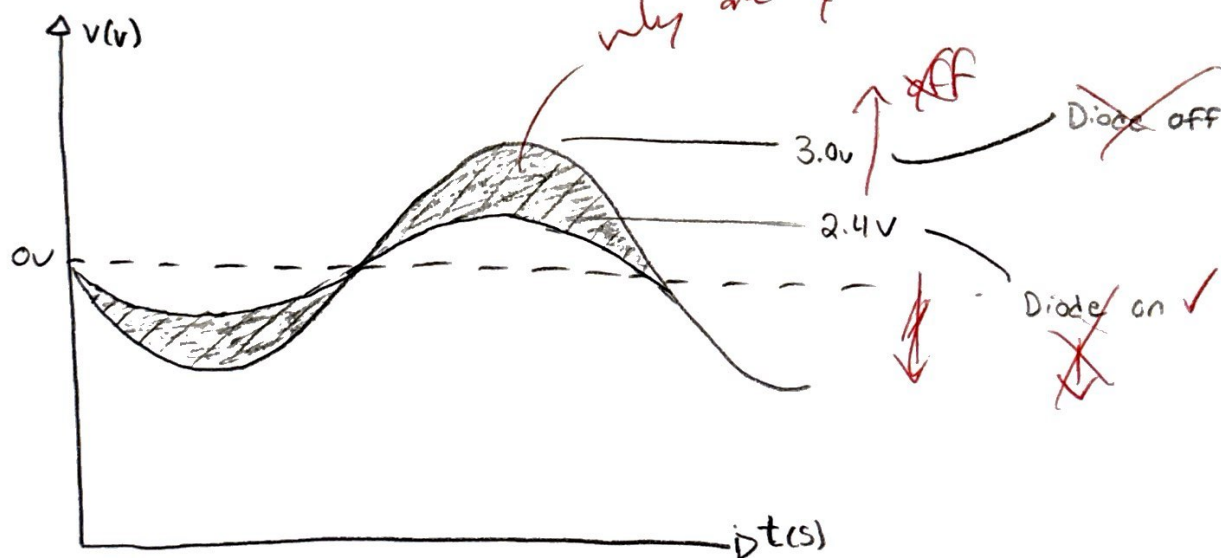

Taylor Carver
Dr. Hoffer
PHYS 351 HW 5
9-9-17

1.22

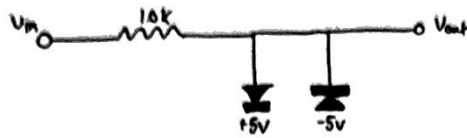

The diodes will only turn on when the respective inputs are $-5.6V$ and $5.6V$ or greater.