
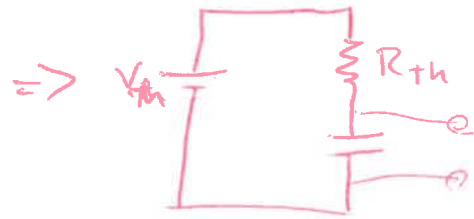


Problem 1.17

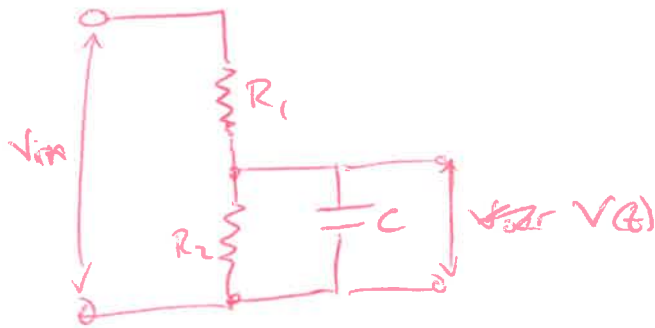

$$R_1 = R_2 = 10 \times 10^3 \Omega \quad C = 0.1 \times 10^{-6} \text{ F}$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{in} = \frac{V_m}{2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{100 \text{ k}}{20 \text{ k}} = 5 \text{ k} = 5000 \Omega$$

$$RC = \frac{5 \times 10^3}{5000} \Omega \times 0.1 \times 10^{-6} \text{ F} = 0.5 \times 10^{-3} \text{ s}$$



Problem 1.18

$$I = C \frac{dV}{dt}$$

$$\int_0^t I dt = C \int_0^{10V} dV$$

$$I t = C 10V$$

$$\text{ex. } 1 \times 10^{-3} t = \frac{1 \times 10^{-6}}{1 \times 10^{-3}} 10$$

$$t = 1 \times 10^{-2} \text{ s}$$

Name: KEY


Electronics for Scientists

RC Circuit

Instructions

Complete the following exercises to the best of your ability.

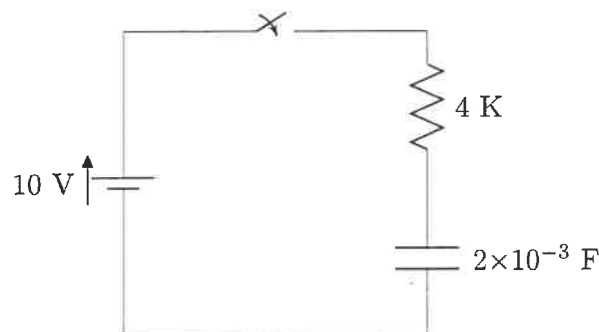A RC circuit has a 10 volt battery, a switch, a 4 K resistor and a 2×10^{-3} F capacitor, as shown below.



$$V_{\text{resistor}} = V_0 e^{-t/RC}$$

$$V_{\text{capacitor}} = V_0 (1 - e^{-t/RC})$$

The capacitor is initially uncharged and the switch is closed at $t = 0$.

$$V = IR$$

1. What is the time constant for this circuit?
2. At a time of 1 time constant after the switch is closed, find the current through the circuit, the voltage across and resistor, and the voltage across the capacitor.
3. At a time of 2 time constant after the switch is closed, find the current through the circuit, the voltage across and resistor, and the voltage across the capacitor.

$$1) \tau = RC = 4 \times 10^3 \Omega \times 2 \times 10^{-3} \text{ F} = 8 \text{ s}$$

$$2) I = I_0 e^{-t/RC} \quad I_0 = \frac{V_0}{R} = \frac{10 \text{ V}}{4 \times 10^3 \Omega} = 2.5 \text{ mA} \quad I = 2.5 \text{ mA} e^{-1} = 9.2 \times 10^{-4} \text{ A}$$

$$V_{\text{resistor}} = V_0 e^{-t/RC} = 10 \text{ V} e^{-1} = 3.68 \text{ V}$$

$$V_{\text{capacitor}} = V_0 (1 - e^{-t/RC}) = 10 \text{ V} (1 - e^{-1}) = 6.32 \text{ V}$$

$$3) I = I_0 e^{-2} = 3.4 \times 10^{-4} \text{ A}$$

$$V_{\text{res}} = 10 \text{ V} e^{-2} = 1.35 \text{ V}$$

$$V_{\text{cap}} = 10 \text{ V} (1 - e^{-2}) = 8.65 \text{ V}$$