

If + input > - input
then output is positive


If - input > + input
then output is negative

Noninverting Amplifier Negative Feedback


$$\begin{aligned} V_{out} &\sim IR_2 - IR_1 = 0 \\ V_{out} &\approx I(R_1 + R_2) \\ V_{out} &\approx \frac{U_{in}}{R_i} (R_1 + R_2) \end{aligned}$$


Vout =
$$V_{in} + V_{in} \stackrel{R_2}{\downarrow} R_i$$

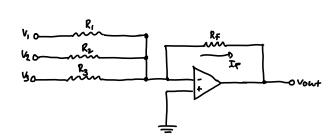 $V_{out} = V_{in} \left(1 + \stackrel{R_2}{\downarrow} R_i \right)$



Inverting summation amplifier

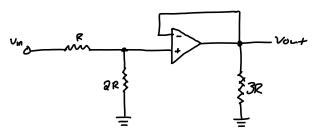

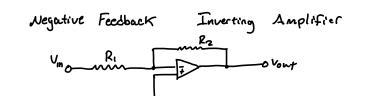

when there is negative Feedback 2 Golden Rules:

-> Inputs do whatever is necessary to make Voltuge difference across inputs Zero


-> Inputs draw no current

Vin - IR, =0

I = VIN/RI

$$V_{int} = -\frac{R_2}{R_1} V_{in}$$

This is called an inverting amplifier.

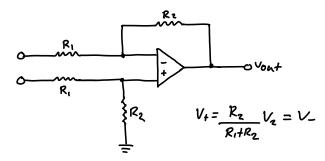

$$V_{1} - IR_{1} = V_{\overline{R}_{2}}$$

$$V_{1} - IR_{1} = \frac{R_{2}}{R_{1} + R_{2}} V_{2}$$


$$\frac{1}{R_{1}} \left(V_{1} - \frac{R_{2} V_{2}}{R_{1} + R_{2}} \right) = I$$

$$V_{0nt} = V_{-} - IR_{2}$$

$$= \frac{R_{1}R_{2}V_{2}}{(R_{1}+R_{2})R_{1}} = \frac{R_{2}}{R_{1}} \left(V_{1} - \frac{R_{2}^{2}V_{2}}{R_{1}+R_{2}}\right)$$

$$= \frac{R_{1}R_{2}V_{2} - R_{2}(R_{1}+R_{2})V_{1} + R_{2}^{2}V_{2}}{R_{1}(R_{1}+R_{2})}$$

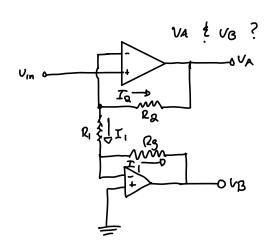Vow =
$$\frac{R_2(R_1+R_2)v_2 - R_2(R_1+R_2)v_1}{R_1(R_1+R_2)}$$



$$V_{IN} - I_{2}R_{2} = VA$$

$$V_{IN} - I_{1}R_{1} - I_{1}R_{3} = VB$$

$$V_{IN} - I_{1}(R_{1} + R_{3}) = VB$$

$$V_{IN} - I_{1}(R_{1} + R_{3}) = VB$$

$$V_{IN} - \frac{V_{iN}}{R_{1}} (R_{1} + R_{3}) = VB$$

$$V_{IN} - V_{iN} - V_{iN} \frac{R_{3}}{R_{1}} = VB$$

$$V_{B} = -\frac{V_{iN} \cdot R_{3}}{R_{1}}$$

$$V_{A} = V_{iN} (1 + \frac{R_{3}}{R_{1}})$$

Va= Vin + Vin R2