
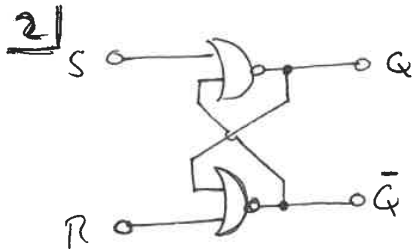


Flip Flops 1 handout

1

A	B	$A+B$
0	0	00
0	1	01
1	0	01
1	1	10

\uparrow \uparrow
 AND XOR
 2^1 2^0

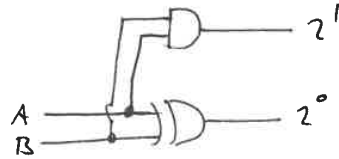

NOR

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Assume Q starts low
and R and S start low
 $\Rightarrow \bar{Q}$ starts high!

S changed to high: Q stays low, \bar{Q} stays high

S changed back to low: Q stays low, \bar{Q} stays high

R changed to high: \bar{Q} goes low, Q goes high.


R changed back to low: \bar{Q} stays low, Q stays high

S changed to high: Q goes low \bar{Q} goes high

so changing R to high saves bit, S resets.

so diagram labeled bad! flip $S \leftrightarrow R$ and acts like

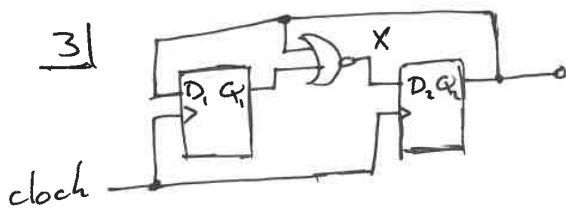our NAND SR latch with changing $0 \rightarrow 1$ doing the action
changing $1 \rightarrow 0$ on NAND creates changes




D	Q
0	0
1	1

\bar{Q} changes on + edge clock!

Assume Q_1 and Q_2 start low

NOR gates flip immediately!

D flop changes based on what D sees!

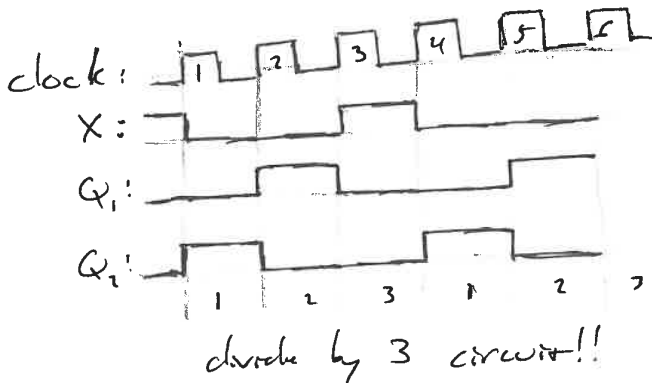

X (NOR) changes immediately when
either Q_1 or Q_2 go high

Q_2 changes dependant on X at
next clock goes +

Q_1 changes dependant on Q_2 at
next clock goes +