

Announcements

□ Homework for tomorrow...

Ch. 30: CQ 11, Probs. 28, 34, & 58

CQ6: $I_a = I_d > I_b = I_c$

30.10: a) $J = 1.7 \times 10^7 \text{ A/m}^2$ b) $i_e = 5.3 \times 10^{18} \text{ s}^{-1}$

30.14: $D = 1.8 \times 10^{-3} \text{ m}$

30.16: $J = 42. \times 10^6 \text{ A/m}^2$

□ Office hours...

MW 10-11 am

TR 9-10 am

F 12-1 pm

□ Tutorial Learning Center (TLC) hours:

MTWR 8-6 pm

F 8-11 am, 2-5 pm

Su 1-5 pm

Chapter 30

Current & Resistance (*Resistance and Ohm's Law*)

Review...

- *Current density related to the E -field...*

$$J = \sigma E$$

- *Resistivity & conductivity...*

$$\rho = \frac{1}{\sigma} = \frac{m}{n_e e^2 \tau}$$

- *Ohm's Law...*

$$I = \frac{\Delta V}{R}$$


where

$$R = \frac{\rho L}{A}$$

Quiz Question 1

Wire 2 has *twice* the length and *twice* the diameter of wire 1. What is the ratio R_2/R_1 of their resistances?


1. $1/4$.
2. $1/2$.
3. 1.
4. 2.
5. 4.

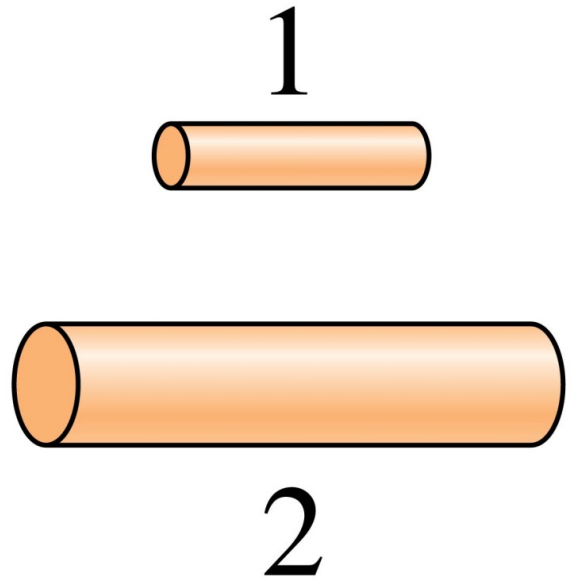

Resistance and Ohm's Law

- A battery is a *source* of potential difference ΔV_{bat} .
- The battery *creates* a potential difference $\Delta V_{\text{wire}} = \Delta V_{\text{bat}}$ between the ends of the wire.
- The potential difference in the wire ΔV_{wire} generates an E -field in the wire.
- The E -field establishes a current $I = JA = \sigma AE$ in the wire.
- The current in the wire is determined *jointly* by the battery and the wire's resistance, R to be:

$$\square I = \Delta V_{\text{wire}}/R$$

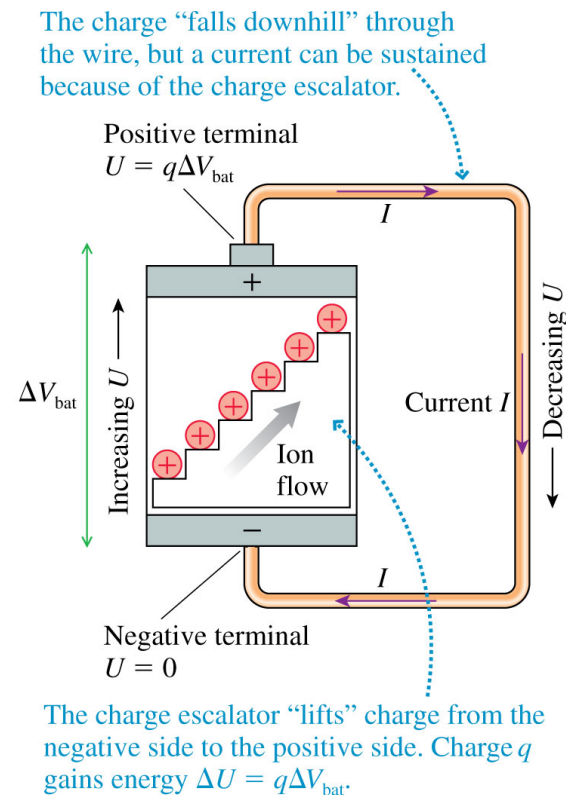


Resistance and Ohm's Law

Notice: Ohm's Law is NOT a Law!

The materials to which Ohm's law applies are called *Ohmic*.


□ i.e.'s: metals and conductors

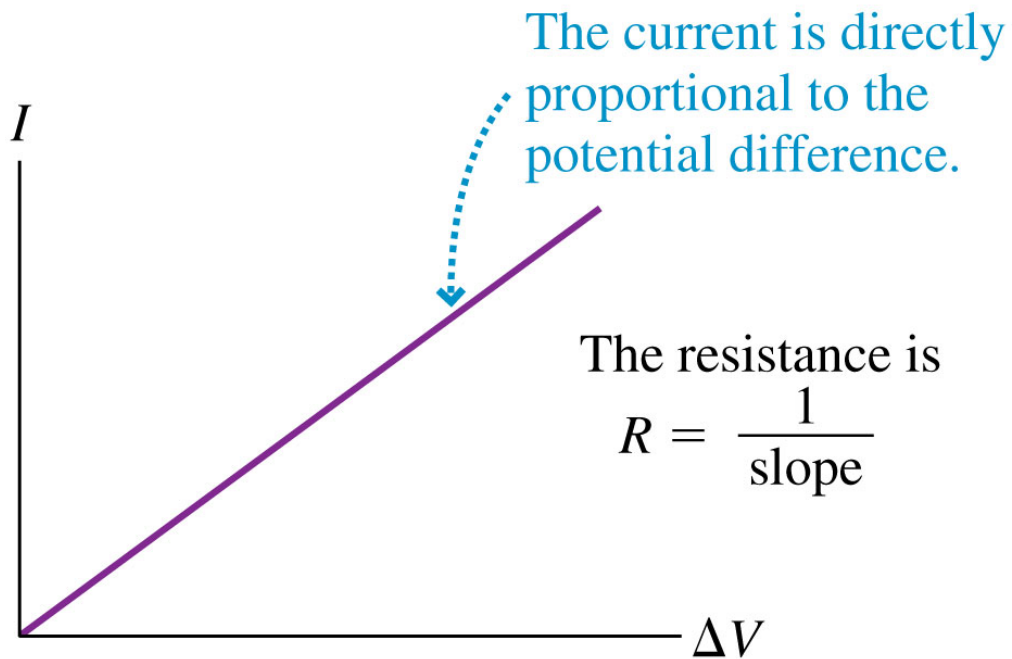

Resistance and Ohm's Law

Nonohmic materials:

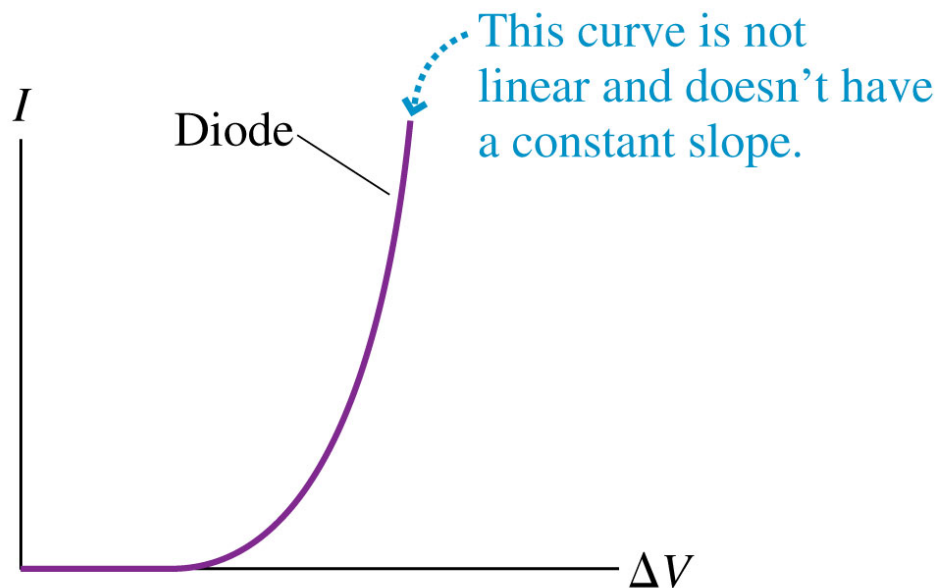
- *current, I* , through the device is *NOT* directly proportional to the *potential difference, ΔV* .
- i.e.'s: diodes, batteries, and capacitors




Quiz Question 2

The current through a wire is measured as the potential difference ΔV is varied.

What is the wire's resistance?

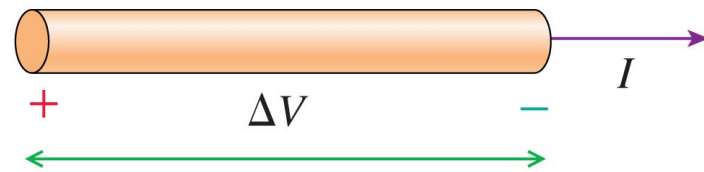


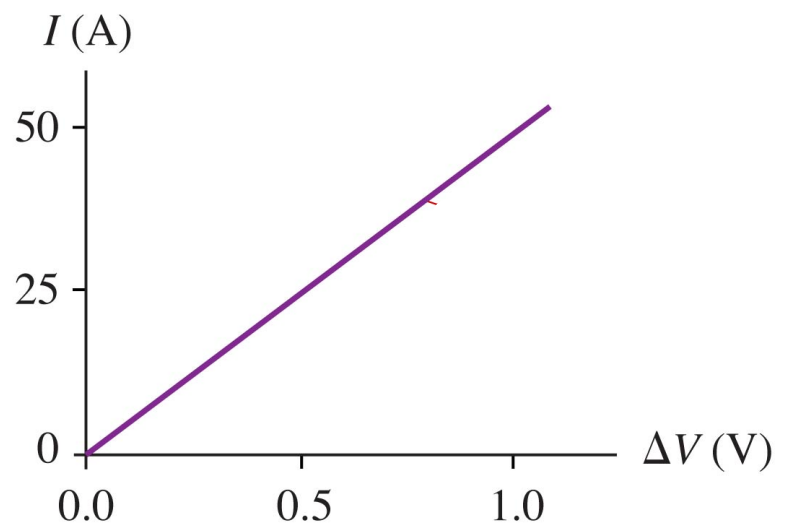1. $0.01\ \Omega$.
2. $0.02\ \Omega$.
3. $50\ \Omega$.
4. $100\ \Omega$.
5. Some other value.



Resistance and Ohm's Law

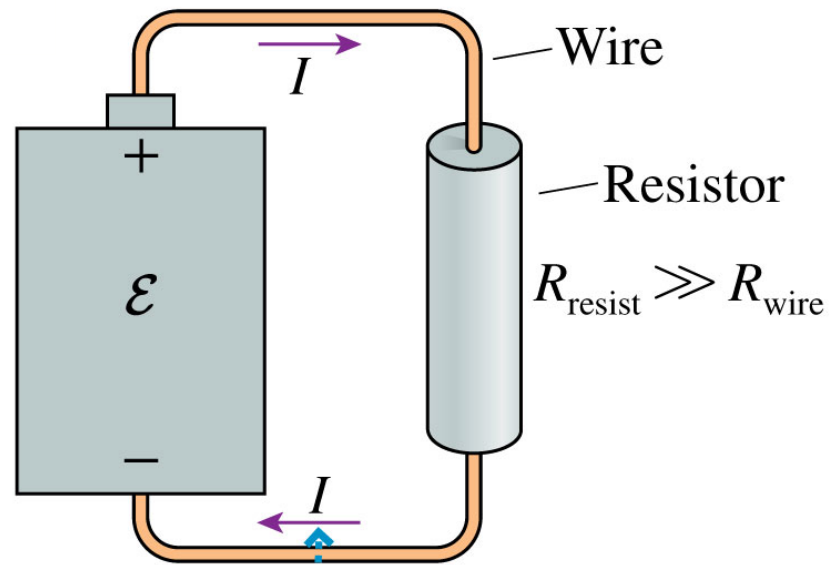Q: How does the voltage drop across the wires compare to the voltage drop across the resistor?




The current is constant along the wire-resistor-wire combination.

Resistance and Ohm's Law

Q: How does the voltage drop across the wires compare to the voltage drop across the resistor?

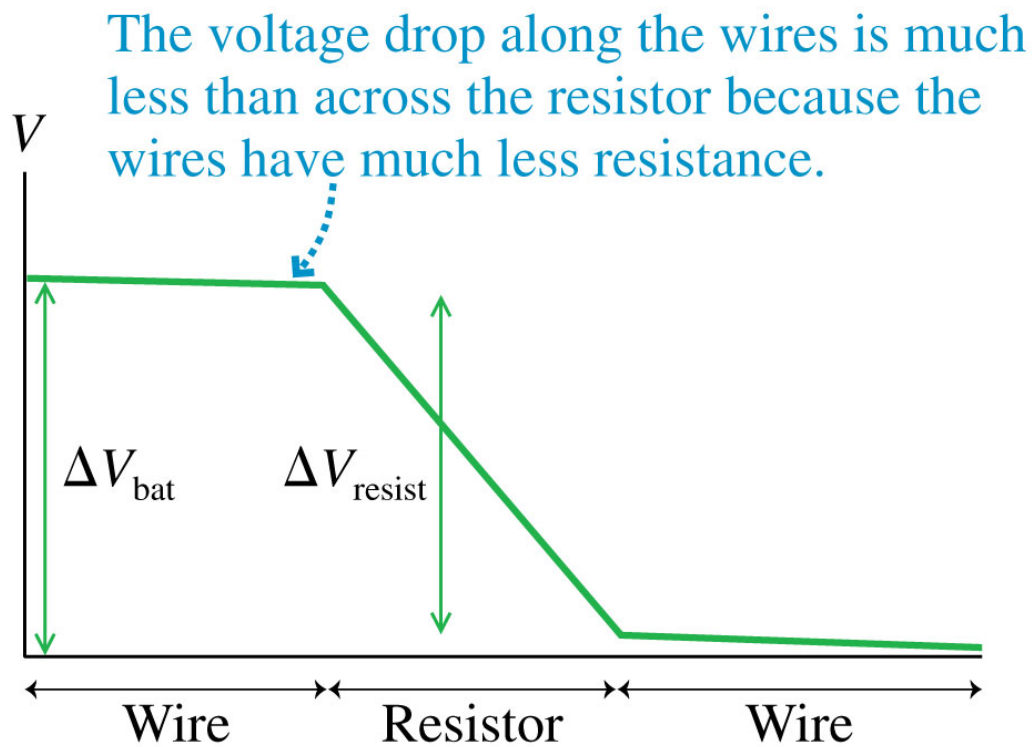A: $\Delta V_{\text{wire}} \ll \Delta V_{\text{resist}}$



i.e. 30.8:

A battery and a resistor

What resistor would have a 15 mA current if connected across the terminals of a 9.0 V battery?