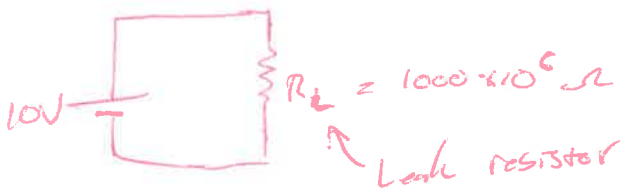


1.9

$$V = IR$$

$$R_L = 10 \times 10^6 \Omega$$




$$V = IR$$

$$10V = I_L R_L$$


$$I_L = \frac{10V}{1000 \times 10^6} \approx 0$$

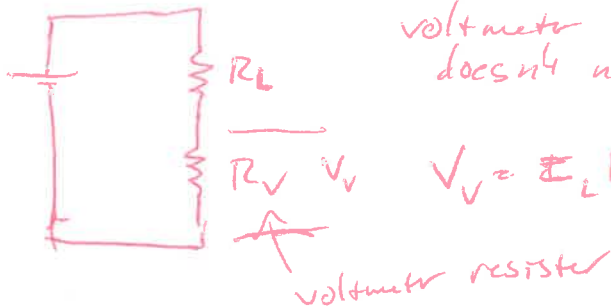because leak resistor is much bigger than voltmeter resistor, attaching in series doesn't noticeably decrease current



$$V_V = I_L R_V = \frac{10V}{1000 \times 10^6} = 0.1 \mu V$$

1.10

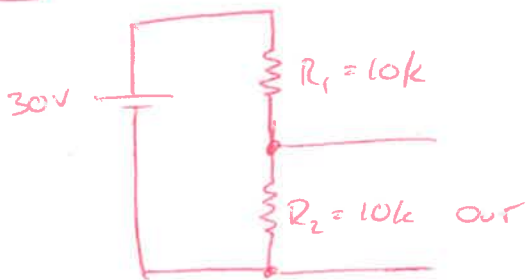

a) No load

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$


b) R_{Load} ($R_2 + R_{Load}$ Parallel) $= R_e = \frac{R_2 R_L}{R_2 + R_L}$

so new voltage divider

$$V_{out} = \frac{R_e}{R_1 + R_e} V_{in} = \frac{\frac{R_2 R_L}{R_2 + R_L}}{R_1 + \frac{R_2 R_L}{R_2 + R_L}} V_{in} = \frac{\frac{R_2 R_L}{R_2 + R_L}}{\frac{R_1 R_2 + R_1 R_L + R_2 R_L}{R_2 + R_L}} V_{in}$$

c) Thevenin $V_{th} = \frac{R_2}{R_1 + R_2} V_{in}$ $R_{th} = \frac{R_1 R_2}{R_1 + R_2}$


$$I = \frac{V}{R}$$

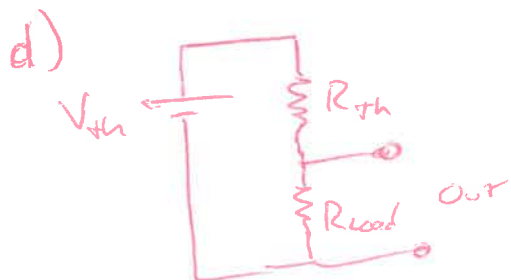

$$V_{out} = \frac{V_{th}}{R_{th} + R_{Load}} = \frac{\frac{R_2}{R_1 + R_2} V_{in}}{\frac{R_1 R_2}{R_1 + R_2} + R_L} = \frac{\frac{R_2}{R_1 + R_2} V_{in}}{\frac{R_1 R_2 + R_1 R_L + R_2 R_L}{R_1 + R_2}}$$

Prashn 1.11

$$P = IV$$

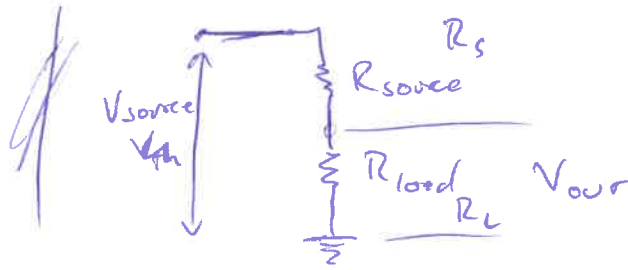

$$P = IV = \frac{V^2}{R}$$

$$\frac{V_{out}^2}{R_{load} (R_L)}$$

$$V_{out} = \frac{R_{load} R_L}{R_{source} + R_L}$$

~~$R_s + R_L$~~

$$P = \frac{R_L^2}{(R_s + R_L)^2} = \frac{R_L}{(R_s + R_L)^2}$$

$$\frac{dP}{dR_L} = \frac{1}{(R_s + R_L)^2} + \frac{R_L(-2)}{(R_s + R_L)^3} = 0$$

$$1 - \frac{2R_L}{R_s + R_L} = 0$$

$$1 = \frac{2R_L}{R_s + R_L}$$

$$R_s + R_L = 2R_L$$

$$\boxed{R_s = R_L}$$