

10.1

To decimal

a) 11101010110_2

$$1 \cdot 2^8 + 1 \cdot 2^5 + 1 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$$

117.

$$0 \cdot 2^{-1} + 1 \cdot 2^{-2} + 1 \cdot 2^{-3} + 0 \cdot 2^{-4}$$

0.375

117.375₁₀ ✓

b) 11.01010101_2

$$1 \cdot 2^1 + 1 \cdot 2^0$$

3

$$0 \cdot 2^{-1} + 1 \cdot 2^{-2} + 0 \cdot 2^{-3} + 1 \cdot 2^{-4} + 0 \cdot 2^{-5} + 1 \cdot 2^{-6} + 0 \cdot 2^{-7} + 1 \cdot 2^{-8}$$

0.332031

3.332031₁₀ ✓

c) $2A_H$ $A=10$

$$2 \cdot (16^1) + 10(16^0)$$

32 + 10

42

42 ✓

convert to hexadecimal

a) 1023_{10}

$$1023/16 = 63 \text{ r } 15 = F$$

$$63/16 = 3 \text{ r } 15 = F$$

$$3/16 = 0 \text{ r } 3$$

3FF₁₆

b) 101110101101_2

$$1 \cdot 2^{11} + 0 \cdot 2^{10} + 1 \cdot 2^9 + 1 \cdot 2^8 + 1 \cdot 2^7 + 0 \cdot 2^6 + 1 \cdot 2^5 + 0 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$$

2989

$$2989/16 = 186 \text{ r } 13 = D$$

$$186/16 = 11 \text{ r } 10 = A$$

$$11/16 = 0 \text{ r } 11 = B$$

BAD₁₆

10.1 continued

C.) 61453_{10}

$$61453_{10} = 3840 \quad r \ 13 = D$$

$$3840_{10} = 240 \quad r \ 0$$

$$240_{10} = 15 \quad r \ 0$$

$$15_{10} = 0 \quad r \ 15 = F$$

Food ₁₆ ✓

10.7

A)



make truth
table!!


This is a nor gate, the output will be high if the input is high, it usually depends on the inputs but there is only one here. This will also invert.

B)




This is an and gate, the output will be high if both inputs are high, there is only one input for this gate.

C)

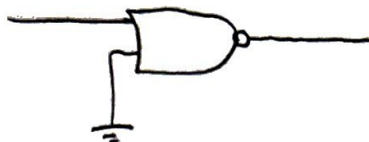

This is a nor gate, the output will be high if one of the inputs is high, since one is tied to ground, the other input just has to be high. This will also invert. No high input, therefore no high output.

D)

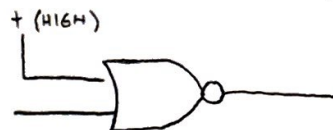


This is a nor gate, since there is a high input, the output of this will be high. The signal in this nor gate will also invert.

E)



This is an and gate, if both the inputs are high, the output will be high. But since that is not the case here, the output will not be high.

F)

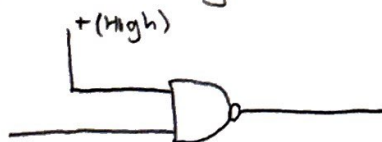

This is an and gate, if both the inputs are high, the output will be high and it will invert. Since only one input is high, the output will not be high and it will not invert.

108


a) Inverter From a NOR 1 input!



b) OR From NOR's



c) OR from NANDs

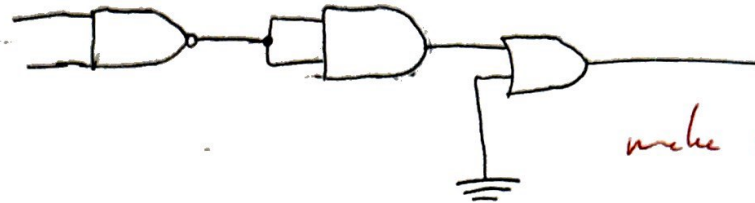

make truth tables!

10 a


a) 3 input $\xrightarrow{\text{from}}$ 2 input




b) 3 input $\xrightarrow{\text{from}}$ 2 input



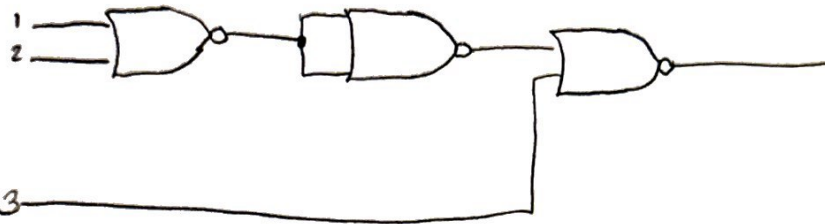c) 3 input $\xrightarrow{\text{from}}$ 2 input



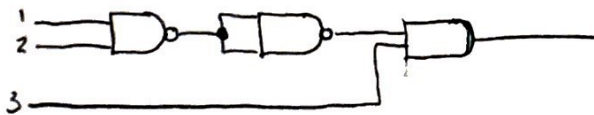d) 3 input $\xrightarrow{\text{from}}$ 2 input



truth tables!!