


Chapter 31

Fundamentals of Circuits *(Circuit Elements and Diagrams & Kirchoff's Laws and the Basic Circuit)*

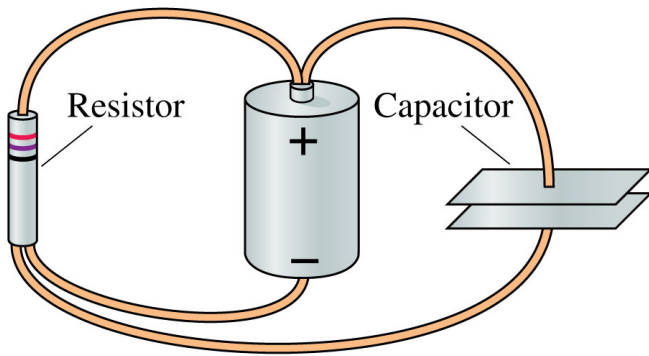31.1:

Circuit Elements and Diagrams


Simple circuit of a resistor and a capacitor connected by wires to a battery.



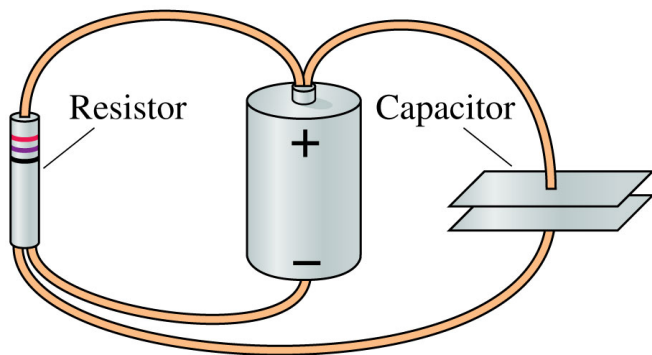
31.1:

Circuit Elements and Diagrams

Simple circuit of a resistor and a capacitor connected by wires to a battery.




Equivalent circuit diagram

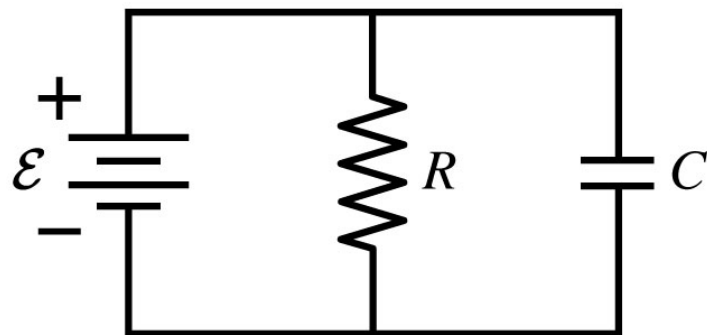

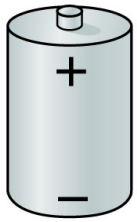31.1: Circuit Elements and Diagrams

Circuit elements with equivalent symbols..




Battery




Wire



Resistor

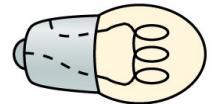



Bulb

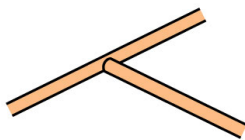

Junction



Capacitor

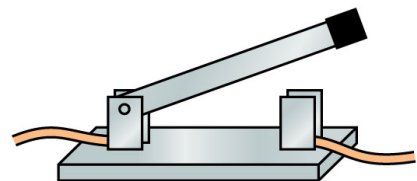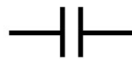

Switch




31.2:

Kirchoff's Laws and the Basic Circuit

For a circuit junction, *Kirchoff's Junction rule* holds...

$$\sum I_{in} = \sum I_{out}$$

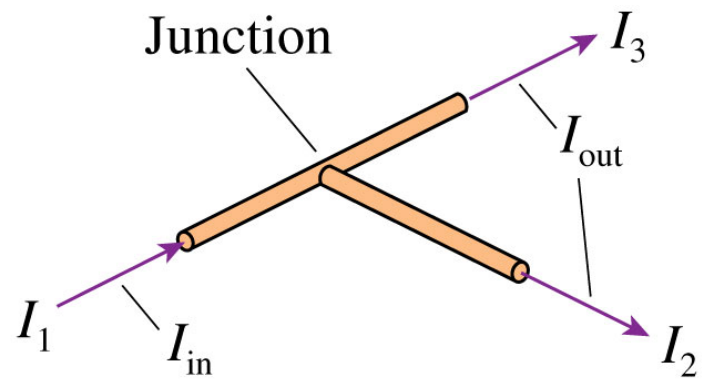


Junction law: $I_1 = I_2 + I_3$

31.2:

Kirchoff's Laws and the Basic Circuit

For a circuit, *Kirchoff's Loop rule* holds...
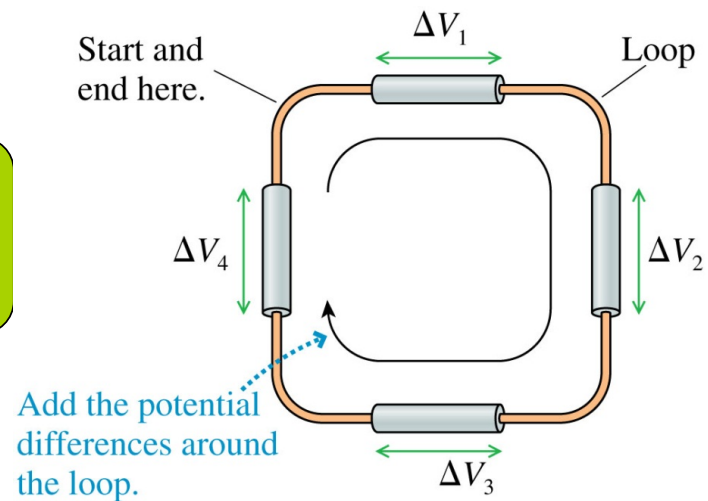
$$\Delta V_{loop} = \sum (\Delta V)_i = 0$$



Loop law: $\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$

31.2:

Kirchoff's Laws and the Basic Circuit


Using *Kirchoff's loop law*...

1. Draw a circuit diagram, labeling quantities.
2. Assign a direction to the current.
3. “Travel” around the loop.
4. Apply the loop law:

$$\sum (\Delta V)_i = 0$$

Quiz Question 1

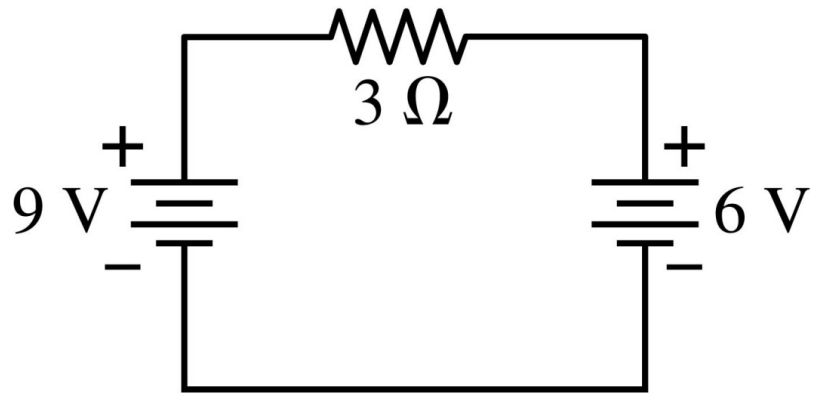The current through the $3\ \Omega$ resistor is



1. 9 A.
2. 6 A.
3. 5 A.
4. 3 A.
5. 1 A.

i.e. 31.1:

Two resistors and two batteries

Analyze the circuit shown in the figure.

- Find the current in and the potential difference across each resistor.
- Draw a graph showing how the potential changes around the circuit, starting from $V = 0\text{V}$ at the negative terminal of the 6 V battery.

