
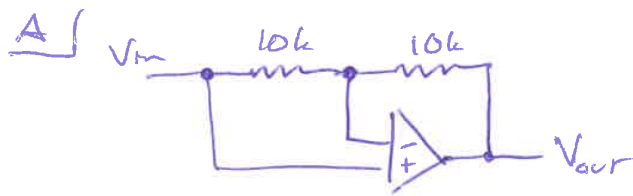


Problem 4.4

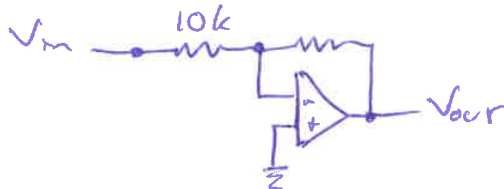

or...




$$V_+ = V_{in} = V_-$$

$$\text{so } V_{in} - IR_1 = V_{in} \quad \text{so } I = 0$$

$$\text{so } V_{in} - I R_2 = V_{out}$$


$$\text{so } V_{out} = V_{in}$$

inverter...

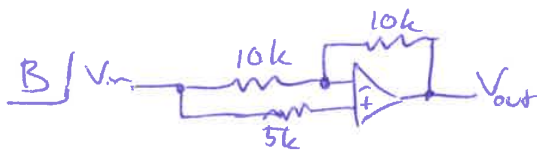


V_+ draws no current... so
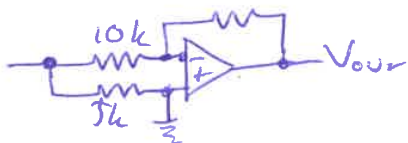
$$V_+ = V_{in} = V_- = V_{out} \quad \text{follower}$$



$V_+ = 0$ so just inverter again

Op Amp handout Problem

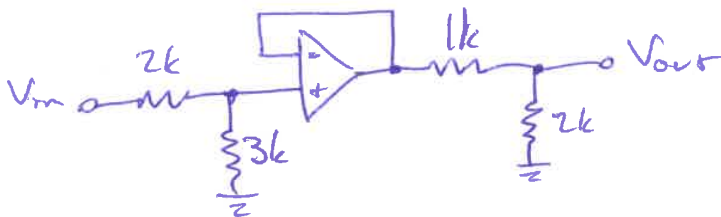

$$V_+ = \frac{3}{3+2} V_{in} = \frac{3}{5} V_{in} = V_-$$

$$V_{out} = \frac{2}{2+1} V_- = \frac{2}{3} V_- = \frac{2}{3} \frac{3}{5} V_{in} = \frac{2}{5} V_{in}$$


$$\text{if } V_{in} = 10V$$

$V_{out} = $	2V	4V
--------------	---------------	----

Problem 4.6

First 1 digit digital to analog

+1V is on, 0V off

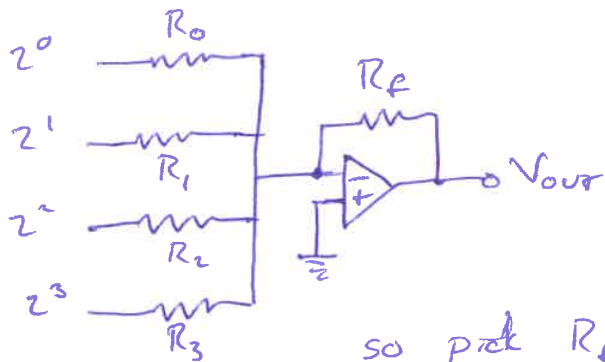

$$\frac{R_f}{R_0} = 1 \quad \frac{R_f}{R_1} = 2 \quad \frac{R_f}{R_2} = 4 \quad \frac{R_f}{R_3} = 8$$


$$\frac{R_f}{R_0} = 1 \quad \frac{R_f}{R_1} = 2 \quad \frac{R_f}{R_2} = 4 \quad \frac{R_f}{R_3} = 8$$

so pick $R_f = 8k$

then $R_0 = 8k$ $R_1 = 4k$ $R_2 = 2k$ $R_3 = 1k$

Now 2 Digit digital to Analog (need to reduce by factor of 10 to stay within +15V supply of opamp)

Same as above, but 4 additional inputs

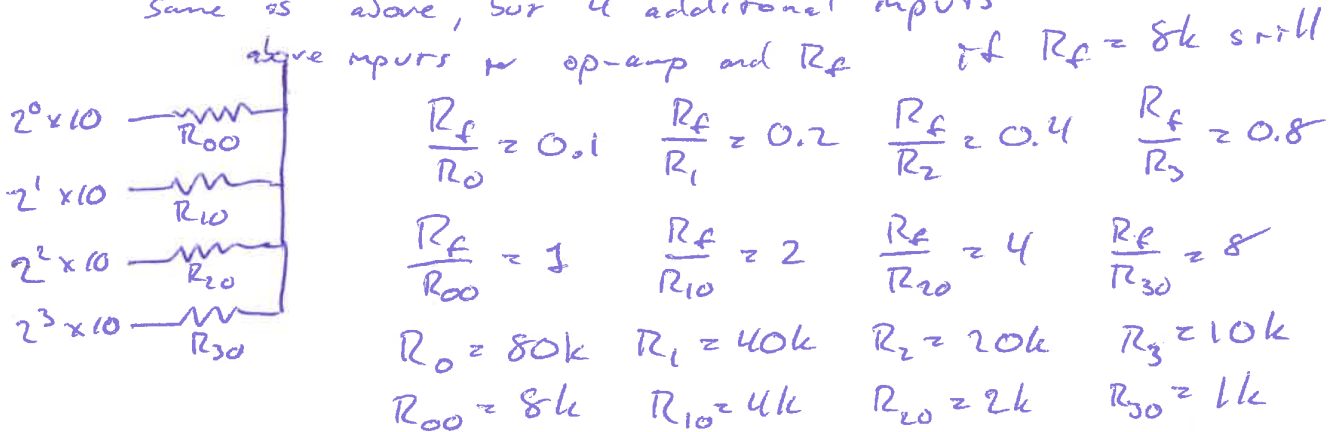

$$\frac{R_f}{R_0} = 0.1 \quad \frac{R_f}{R_1} = 0.2 \quad \frac{R_f}{R_2} = 0.4 \quad \frac{R_f}{R_3} = 0.8$$

$$\frac{R_f}{R_{00}} = 1 \quad \frac{R_f}{R_{10}} = 2 \quad \frac{R_f}{R_{20}} = 4 \quad \frac{R_f}{R_{30}} = 8$$

$R_0 = 80k$ $R_1 = 40k$ $R_2 = 20k$ $R_3 = 10k$

$R_{00} = 8k$ $R_{10} = 4k$ $R_{20} = 2k$ $R_{30} = 1k$

Now 1 digit to Analog that where on is +5V instead of +1V like Problem 4.6

$$\frac{R_f}{R_0} = \frac{1}{5} \quad \frac{R_f}{R_1} = \frac{2}{5} \quad \frac{R_f}{R_2} = \frac{4}{5} \quad \frac{R_f}{R_3} = \frac{8}{5}$$

if $R_f = 8k$ still

$R_0 = 40k$ $R_1 = 20k$ $R_2 = 10k$ $R_3 = 5k$