
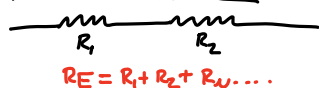


Resistors in Series

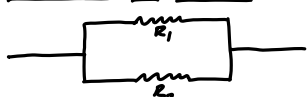

$$R_E = R_1 + R_2 + R_3 \dots$$

Resistors in Parallel




$$R_E = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots}$$


Capacitors: (series) and (parallel)

$$Q = CV \quad I = C \frac{dV}{dt}$$

Series

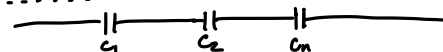

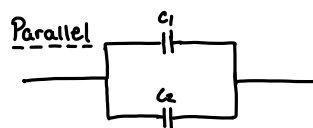
$$C_{EQ} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_n}}$$



$$C_{EQ} = C_1 + C_2$$

Differentiator (differentiates signal)

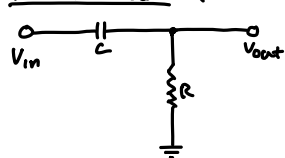


$$I = C \frac{dV}{dt} (V_{in} - V_{out}) = \frac{V_{out}}{R}$$

$$V_{out}(t) = RC \frac{dV_{in}(t)}{dt}$$

$$\frac{dV_{out}}{dt} \ll \frac{dV_{in}}{dt}$$

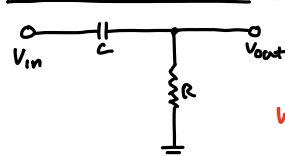
RC Highpass Filter (Blocks low f, passes high f)




$$V_{out} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} V_{in}$$

$$\omega = 2\pi f \quad R = \text{Resistance} \quad C = \text{Capacitance}$$

Transistors

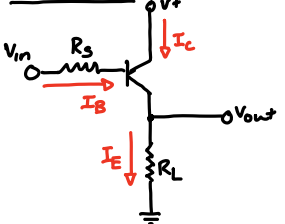


Negative Feedback

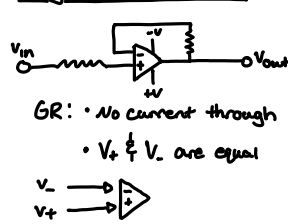


- GR: No current through inputs
- $V_+ \neq V_-$ are equal

Positive Feedback

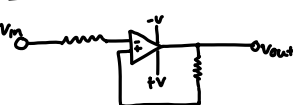

- GR do not apply
- This is where to calculate trigger points, w/ current loops
- Output will try to go between $(V_-) \neq (V_+)$


Sinusoidal Signal

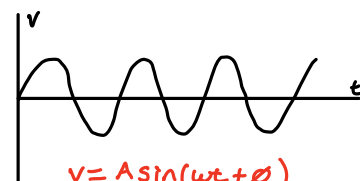

$$V = A \sin(\omega t + \phi)$$

$$\omega = 2\pi f \quad \phi = \text{constant}$$

RC Circuits

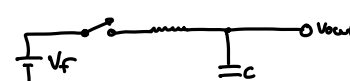


$$I = C \frac{dV}{dt} \quad V_f \equiv V_{out}$$

$$V_{out} = V_f + A e^{-t/\tau}$$

$$V_{out} = V_f (1 - e^{-t/\tau})$$

$$\tau = RC \log_e \left(\frac{V_f}{V_f - V_{out}} \right)$$

Diodes

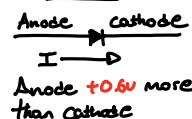

Anode +0.6V more than cathode

Decibels

$$dB = 10 \log_{10} \frac{P_2}{P_1}$$

$$P = \text{Power}$$

$$dB = 20 \log_{10} \frac{A_2}{A_1}$$


$$A = \text{Amplitude}$$

Input & Output Impedance

$$Z_{out} = \frac{Z_s}{\beta} \quad Z_{in} = \beta(Z_c)$$

$$I_E \neq I_C = \beta I_B$$

Oscillators

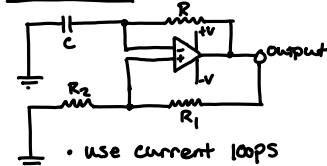

- Use current loops
- Positive side trigger points
- Negative side is RC circuit

Digital Logic

Hex: 0123456789ABCDEF₁₆

Dec: 012345678910₁₀

Bin: 1010110011000...₂

Ex:

Hex → Dec:

$$2C3_{16} \rightarrow 2 \cdot 16^2 + 12 \cdot 16^1 + 3 \cdot 16^0 = 707_{10}$$

Dec → Hex:

$$707_{10} \rightarrow \frac{707}{16} = 44 \quad \frac{44}{16} = 2 \quad \frac{2}{16} = 0$$

$$2C3_{16}$$

Ex:

Bin → Dec:






$$101_2 \rightarrow 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0 = 5_{10}$$

Dec → Bin:


$$5_{10} \rightarrow \frac{5}{2} = 2 \quad \frac{2}{2} = 1 \quad \frac{1}{2} = 0$$

$$101_2$$

Logic Gates

A	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q
0	1	0	0	1	0	0	1	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1	0	0	1	0	1	0	0	1	0
0		1	0	1	1	0	0	1	1	1	0	1	1	1	0	1
NOT																
		NAND		NOR		XOR		AND		OR						

D Flip Flop

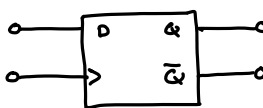

D	Q	Q-bar
0	0	1
1	1	0