

Announcements

▣ Homework for tomorrow...

Ch. 31: CQ 10, Probs. 20, 22, & 46

CQ3: $\Delta V_{12} = 3V$

31.1: See whiteboard

31.6: 8V, 22V

31.8: (48/25)W, (72/25)W

▣ Office hours...

MW 10-11 am

TR 9-10 am

F 12-1 pm

▣ Tutorial Learning Center (TLC) hours:

MTWR 8-6 pm

F 8-11 am, 2-5 pm

Su 1-5 pm

Chapter 31

Fundamentals of Circuits (*Real Batteries & Parallel Resistors*)

Review...


Resistors in *series*....

$$R_{eq} = R_1 + R_2 + \dots$$

Terminal voltage across a *real* battery...

$$\Delta V_{bat} = \mathcal{E} - Ir \leq \mathcal{E}$$

31.5: Real Batteries

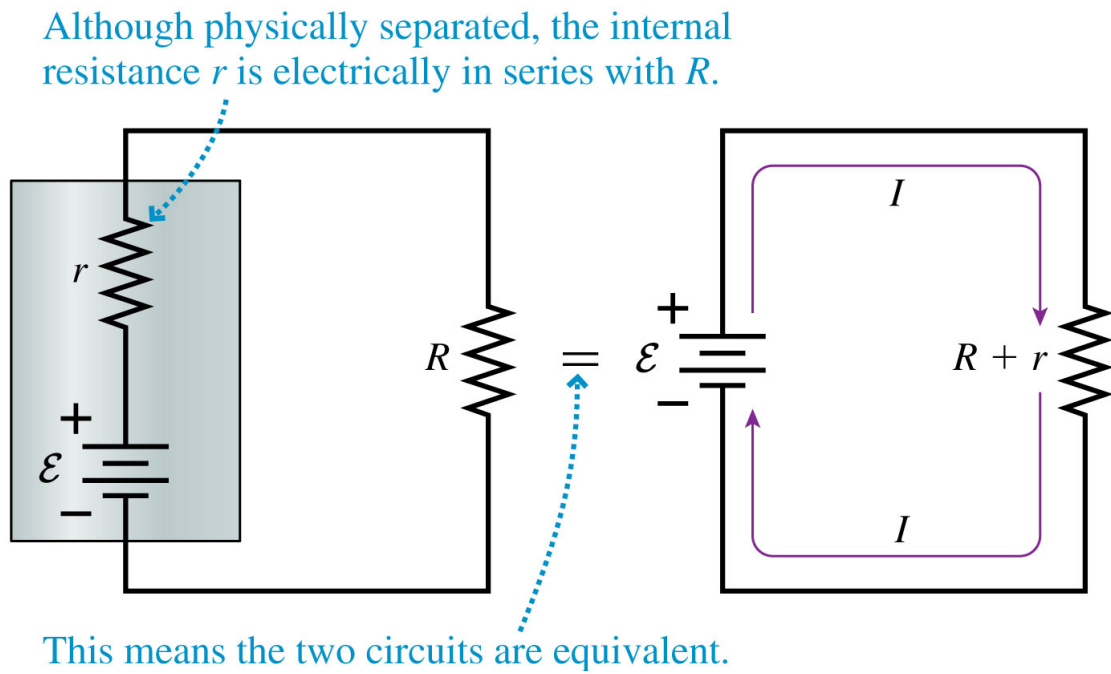

Notice:

$$\Delta V_R = \Delta V_{bat} \text{ , } \Delta V_R \neq \mathcal{E}$$

i.e. 31.6:


Lighting up a flashlight

A 6.0Ω flashlight bulb is powered by a 3.0V battery with an internal resistance of 1.0Ω .

What are the power dissipation of the bulb and the terminal voltage of the battery?

A Short Circuit...

What is the current in this circuit?

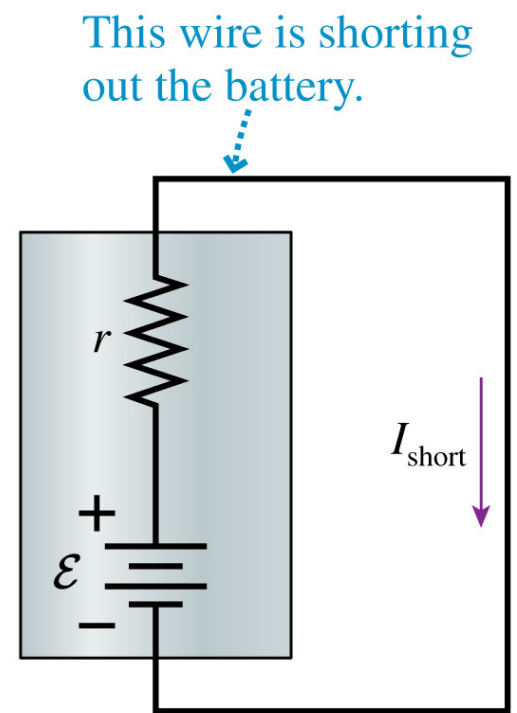


A Short Circuit...

What is the current in this circuit?

$$I_{short} = \frac{\mathcal{E}}{r}$$

Notice:

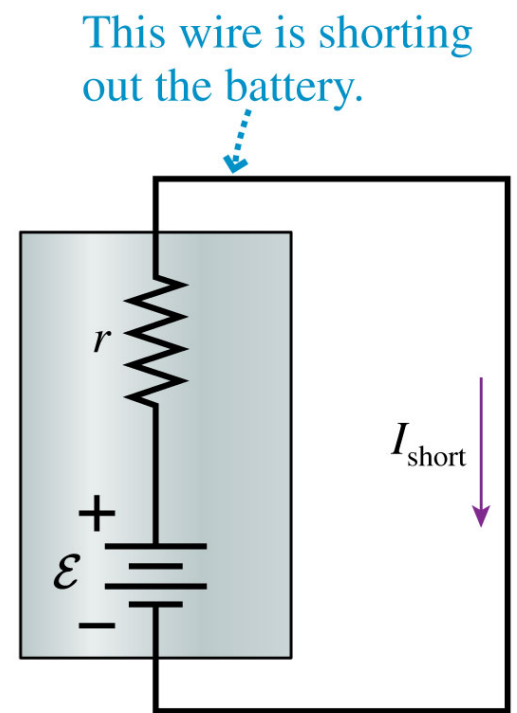This is the *maximum possible current* that this battery can produce!



i.e. 31.7:

A short-circuited battery

What is the short-circuit current of a 12V car battery with an internal resistance of 0.020Ω ?


What happens to the power supplied by the battery?

Quiz Question 1

Consider the circuit below, where the switch is open. The current is the same through bulbs A and B, and they are equally bright. Bulb C is not glowing.

The switch is now closed, what happens to the brightness of A?

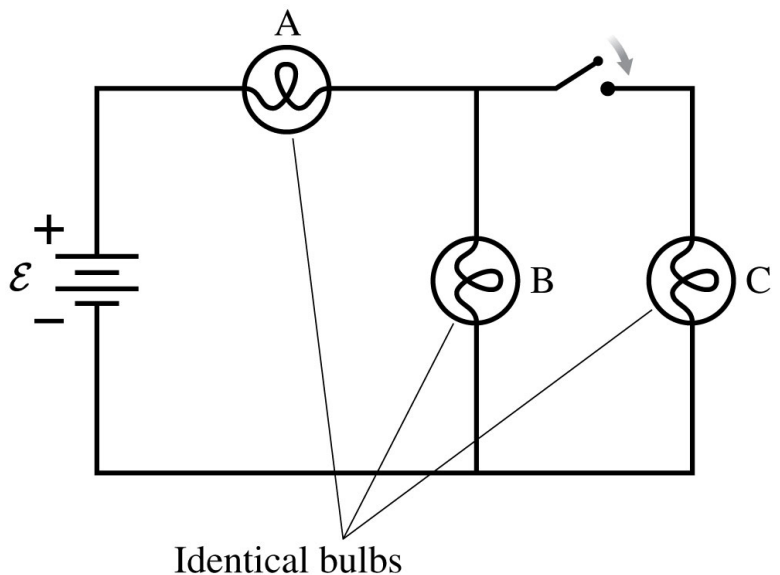
1. It increases.
2. It decreases.
3. It stays the same.



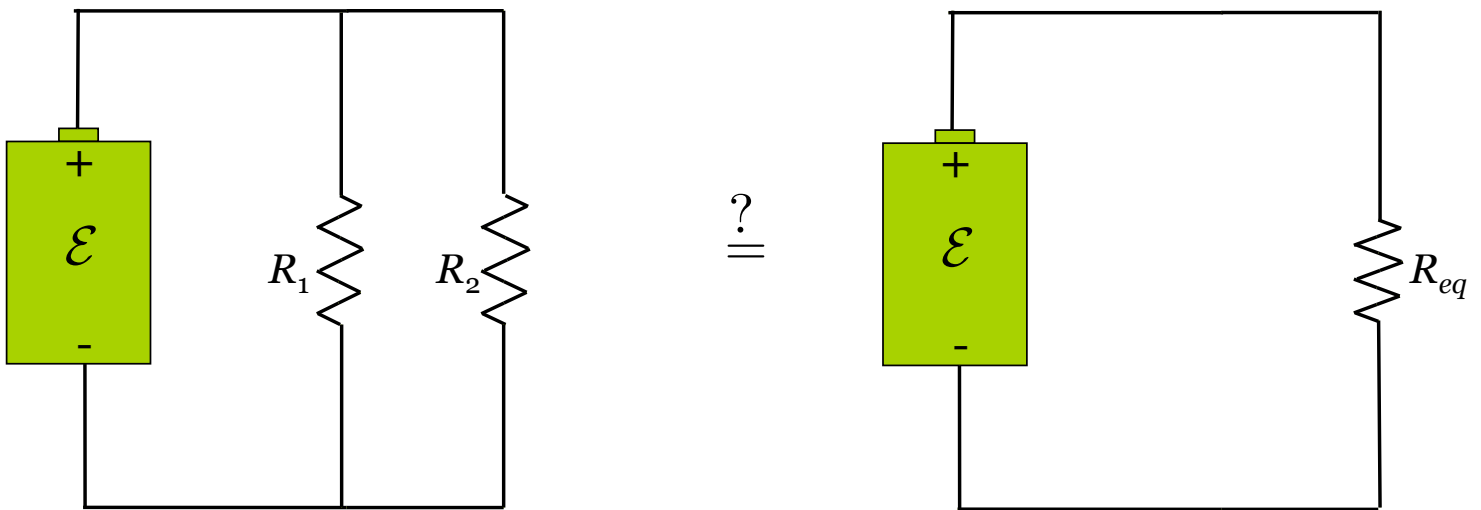31.6: Parallel Resistors

Consider two resistors in *parallel*...


- Can we find an *equivalent resistor*, R_{eq} , to the two resistors, R_1 & R_2 ?



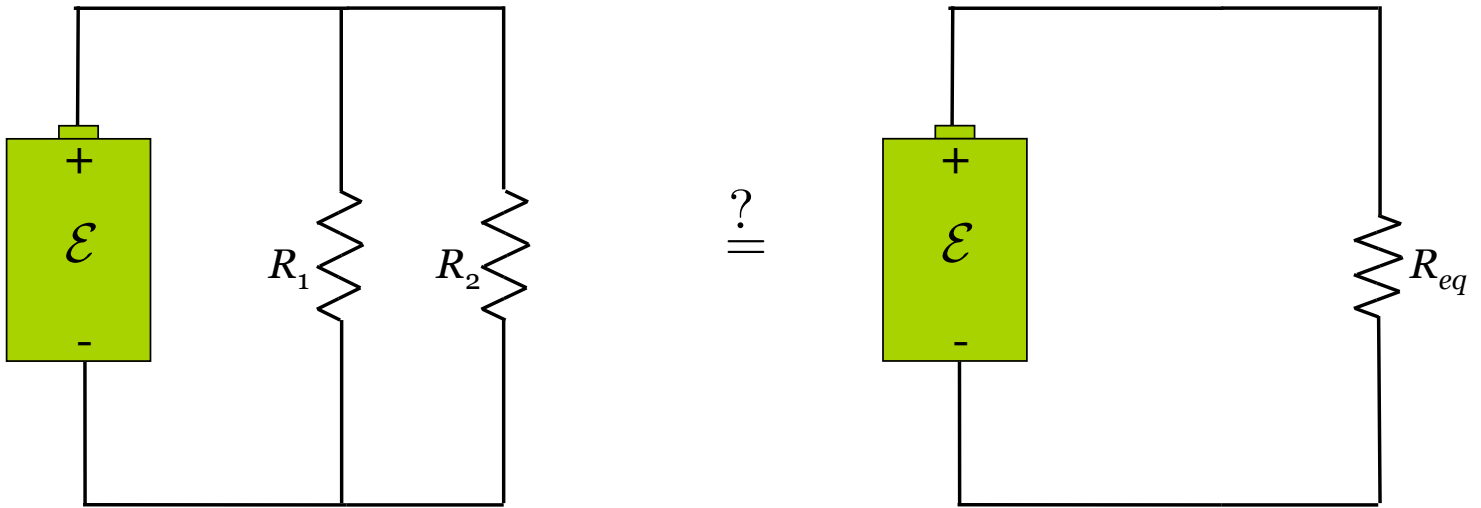31.6: Parallel Resistors

Consider two resistors in *parallel*...

- Can we find an *equivalent resistor*, R_{eq} , to the two resistors, R_1 & R_2 ?




- YES!

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

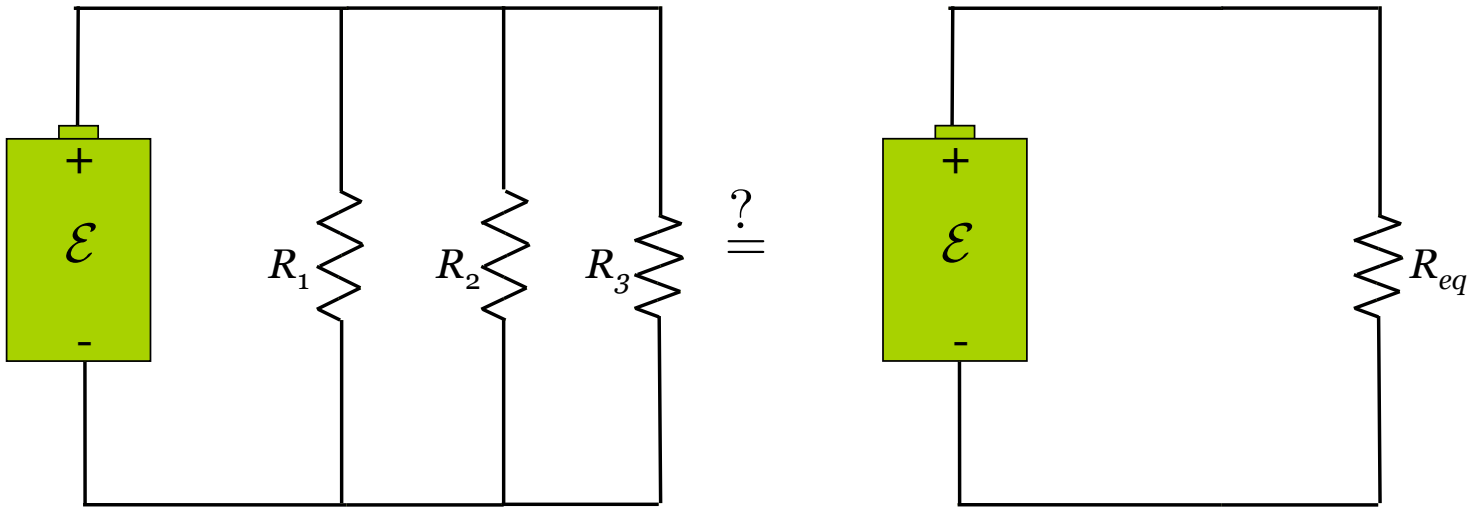31.6: Parallel Resistors

What about several resistors in *parallel*...


- Can we find an *equivalent resistor*, R_{eq} , to the the resistors, R_1, R_2, \dots (all in *parallel*)?



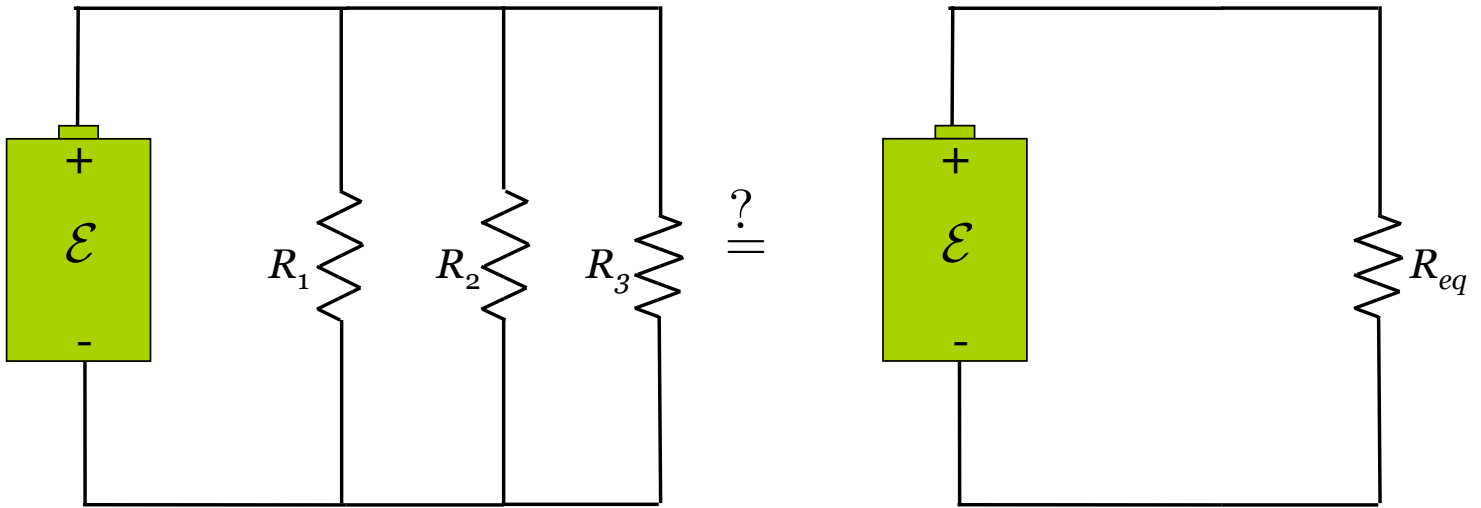31.6: Parallel Resistors

What about several resistors in *parallel*...

- Can we find an *equivalent resistor*, R_{eq} , to the the resistors, R_1, R_2, \dots (all in *parallel*)?



- YES!


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

Quiz Question 1, continued..

Consider the circuit below, where the switch is open. The current is the same through bulbs A and B, and they are equally bright. Bulb C is not glowing.

The switch is now closed, what happens to the brightness of A?

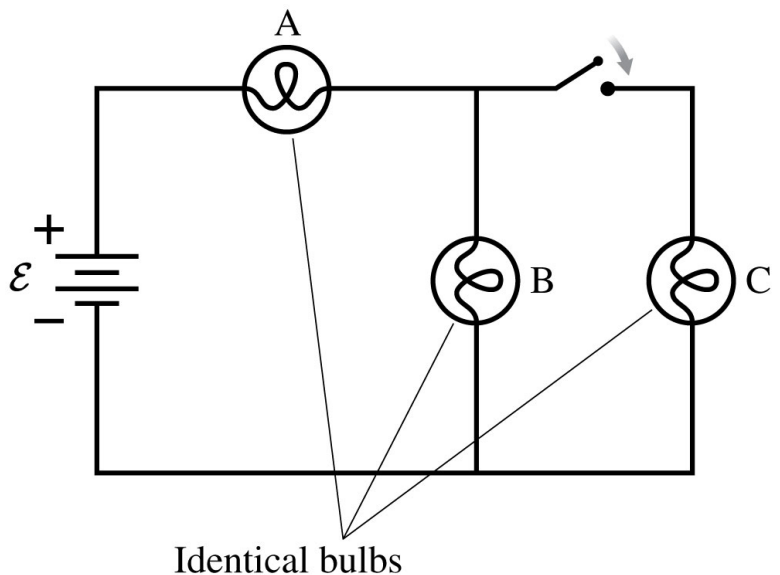
1. It increases.
2. It decreases.
3. It stays the same.



Quiz Question 2

The battery current I is

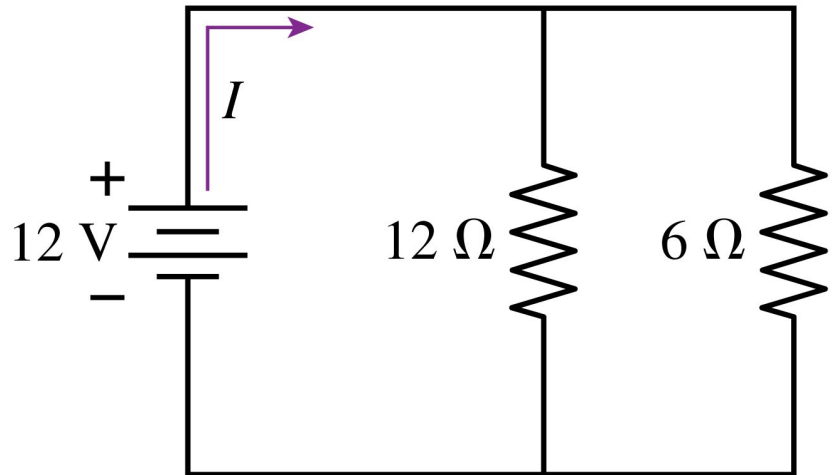
1. 3 A.
2. 2 A.
3. 1 A.
4. $\frac{2}{3}$ A.
5. $\frac{1}{2}$ A.



Quiz Question 3

When the switch closes, the battery current

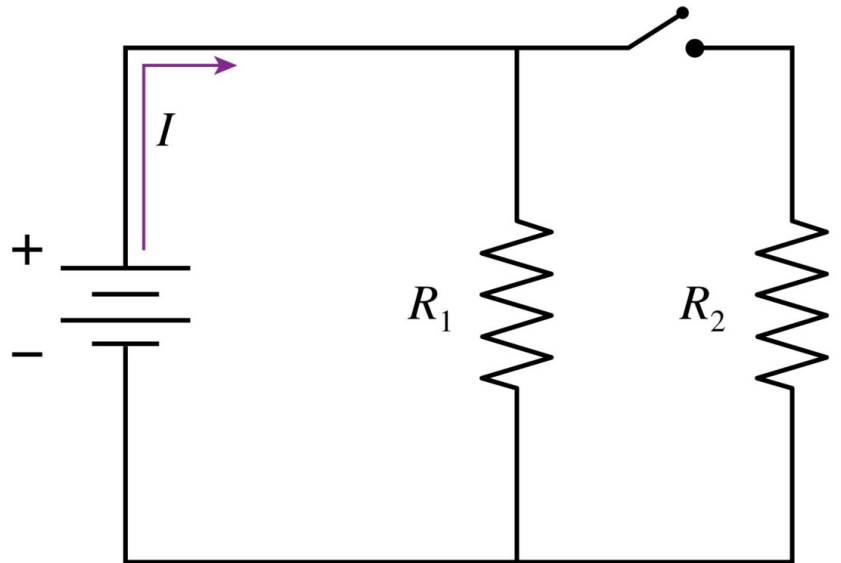
1. increases.
2. stays the same.
3. decreases.



Quiz Question 3

When the switch closes, the battery current

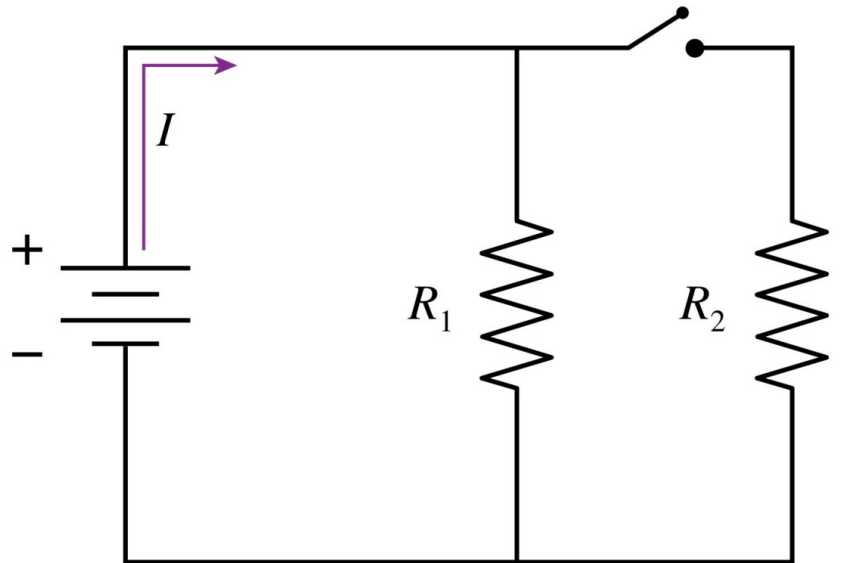1. increases.
2. stays the same.
3. decreases.



Notice:

The equivalent of several resistors in parallel is *always less than* any single resistor in the group.