

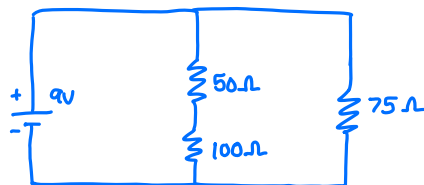


## Problems

31.P.1

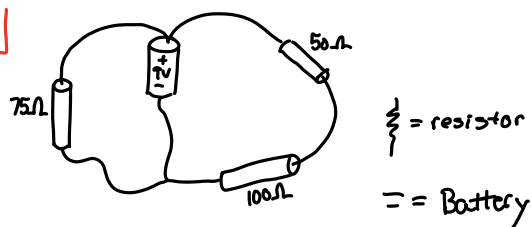

31.P.6

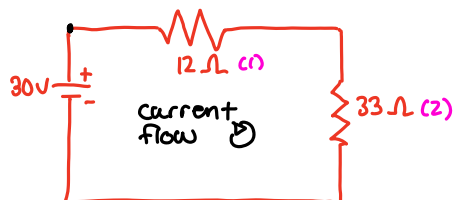

$$\begin{aligned} -I(12\Omega) - I(33\Omega) &= 30V \\ -I(45\Omega) &= 30V \\ I &= -0.66A \\ |I| &= 0.66A \end{aligned}$$

$$\begin{aligned} (1): I &= \frac{\Delta V}{R} \therefore \Delta V = IR \\ R_1 &= 12\Omega \quad \Delta V_1 = (0.66A)(12\Omega) \\ I_1 &= 0.66A \quad \Delta V_1 = 8V \end{aligned}$$


$$\begin{aligned} \Delta V_1 + \Delta V_2 &= \Delta V \\ 8V + 22V &= 30V \end{aligned}$$

$$\begin{aligned} \Delta V_1 &= 8V \\ \Delta V_2 &= 22V \end{aligned}$$

$$\begin{aligned} (2): I &= \frac{\Delta V}{R} \therefore \Delta V = IR \\ R_2 &= 33\Omega \quad \Delta V_2 = (0.66A)(33\Omega) \\ I_2 &= 0.66A \quad \Delta V_2 = 22V \end{aligned}$$

$$30V = 30V \checkmark$$

31.P.8

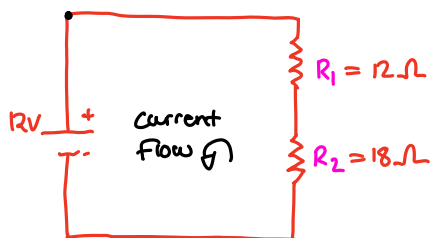

$$\begin{aligned} -I(12\Omega) - I(18\Omega) &= 12V \\ -I(30\Omega) &= 12V \\ I &= -0.4A \\ |I| &= 0.4A \end{aligned}$$

$$\begin{aligned} P_1 &= 1.92W \\ P_2 &= 2.88W \end{aligned}$$

$$\begin{aligned} P &= I^2 R \\ P &= I \Delta V_R \\ P &= \frac{\Delta V_R^2}{R} \end{aligned}$$

$$\begin{aligned} R_1: P &= I_1^2 R_1 \quad P = (0.4A)^2 (12\Omega) \\ I &= 0.4A \quad P = 1.92W \\ R &= 12\Omega \end{aligned}$$

$$\begin{aligned} R_2: P &= I_2^2 R_2 \quad P = (0.4A)^2 (18\Omega) \\ I &= 0.4A \quad P = 2.88W \\ R &= 18\Omega \end{aligned}$$

## Conceptual

31.C.3

The potential difference when the switch is broken is equal to the potential difference of the battery which is 3V

$$\Delta V_{1 \rightarrow 2} = 3V$$