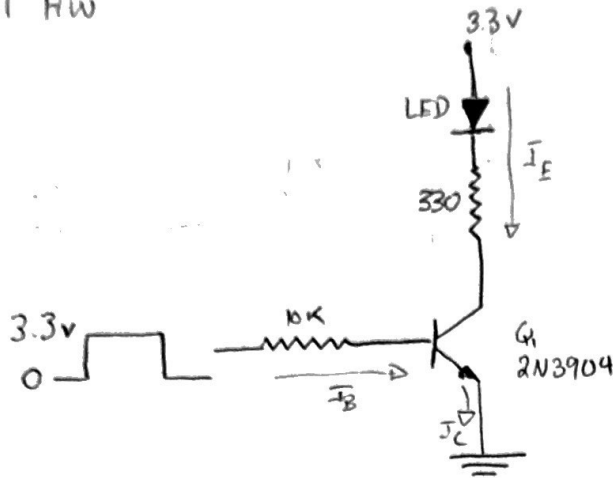


2.1

3/3



$$I_C = I_B + I_E$$

a) loop 1:

$$3.3V - 0.6V - I_E(330) = 3.19V$$

$$2.7V - I_E(330) = 3.19V$$

$$I_E(330) = 0.49V$$

$$I_E = 1.4mA$$

loop 2:

$$3.3V - I_B(10k) = 3.19V$$

$$I_B(10k) = 0.11V$$

$$I_B = 1.1 \times 10^{-5} A$$

$$I_C = 1.5mA$$

$I_C$

$$I_{LED} = 1.4mA$$

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

b)  $\beta$ ?

$$V_{out} = \frac{\beta R_2}{R_1 + \beta R_2} V_{in}$$

$$V_{out} = 3.19V$$

$$\frac{V_{out}}{V_{in}} = \frac{\beta R_2}{R_1 + \beta R_2}$$

$$\frac{V_{out}}{V_{in}} R_1 = \beta R_2 \left( \frac{1}{R_1} - \frac{V_{out}}{V_{in}} \right)$$

$$\frac{V_{out}}{V_{in}} (R_1 + \beta R_2) = \beta R_2$$

$$\frac{\frac{V_{out}}{V_{in}}}{\frac{1}{R_1} - \frac{V_{out}}{V_{in}}} = \beta R_2$$

$$\beta = \frac{\frac{R_1 V_{out}}{V_{in}} - 1}{R_2}$$

$$\frac{V_{out}}{V_{in}} R_1 + \frac{V_{out}}{V_{in}} \beta R_2 = \frac{\beta R_2}{R_1}$$

$$\frac{\frac{V_{out}}{V_{in}}}{\frac{1}{R_1}} - 1 = \beta R_2$$

$$\beta = \frac{\frac{330(3.19V)}{3.3} - 1}{10k}$$


$$\frac{V_{out}}{V_{in}} R_1 = \frac{\beta R_2}{R_1} - \beta R_2 \frac{V_{out}}{V_{in}}$$

$$\frac{R_1 V_{out}}{V_{in}} - 1 = \beta R_2$$

$$\beta = 100$$

2.4

$Z_{out}$  must be  $< Z_{in}$

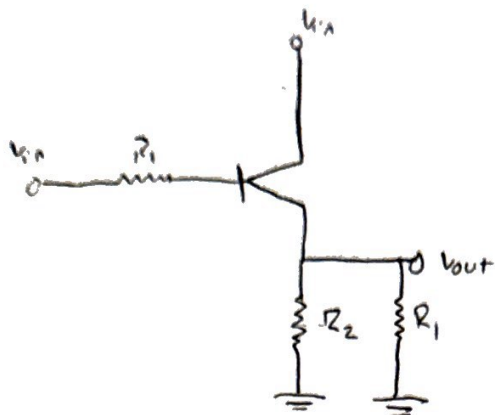

To make sure the output is as close to the input as possible, the  $\beta$  factor must be introduced to compensate for the new resistance.

$$\Delta I_E = \Delta V_B / R$$


$$\Delta I_B = \frac{1}{\beta + 1} \Delta I_E = \frac{\Delta V_B}{R(\beta + 1)} \quad \frac{\Delta V_E}{R_{source}}$$

$$R(\beta + 1) = \frac{\Delta V_B}{\Delta I_B}$$

$$R(\beta + 1) = r_{in}$$

$$Z_{in} = (\beta + 1) Z_{out}$$

25

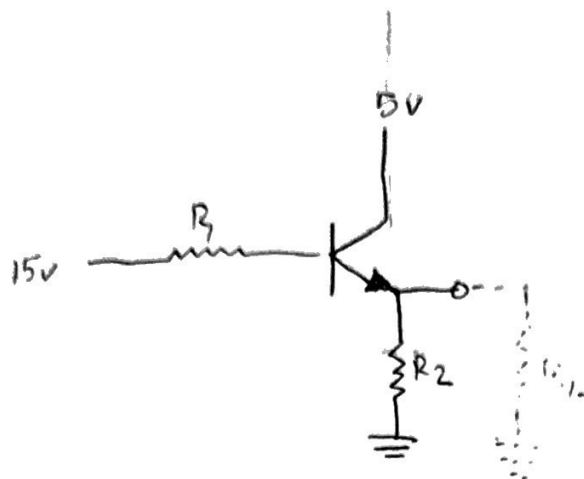

$$R_1 = 95$$

$$R_2 = 10k$$

With such a big difference in the R's,  
the  $V_{out}$  should be right about what  
 $V_{in}$  is. which is 15V.

